

Unijunction Transistor (UJT) & Programmable Unijunction Transistor(PUT)

Unijunction Transistor (UJT)

- Although first introduced in 1948, the device did not become commercially available until 1952.
- The *low cost per unit* combined with the *excellent characteristics* of the device have warranted its use in a wide variety of applications, including “oscillators, trigger circuits, sawtooth generators, phase control, timing circuits, bistable networks, and voltage- or current-regulated supplies”.
- The fact that this device is, in general, a **low-power-absorbing** device under normal operating conditions is a tremendous aid in the continual effort to design relatively efficient systems.

Programmable Unijunction Transistor(PUT)

- The programmable unijunction transistor (PUT) is actually a type of thyristor and not like the UJT at all in terms of structure.
- The only similarity to a UJT is that the PUT can be used in some oscillator applications to **replace the UJT**.
- The PUT is similar to an SCR except that **its anode-to-gate** voltage can be used to both turn on and turn off the device.

Unijunction Transistor (UJT)


UNIUNCTION TRANSISTOR (UJT)

- The unijunction transistor **does not belong** to the thyristor family because it **does not have a four-layer** type of construction.
- The term “unijunction” refers to the fact that the UJT has a **single pn junction**.
- The UJT is useful in certain oscillator applications and as a triggering device in thyristor circuits.
- It is a three-terminal device whose basic construction is shown in Figure 2–1(a). The schematic symbol appears in Figure 2–1(b).


UNIJUNCTION TRANSISTOR (UJT)

► FIGURE 2-1

The unijunction transistor (UJT).

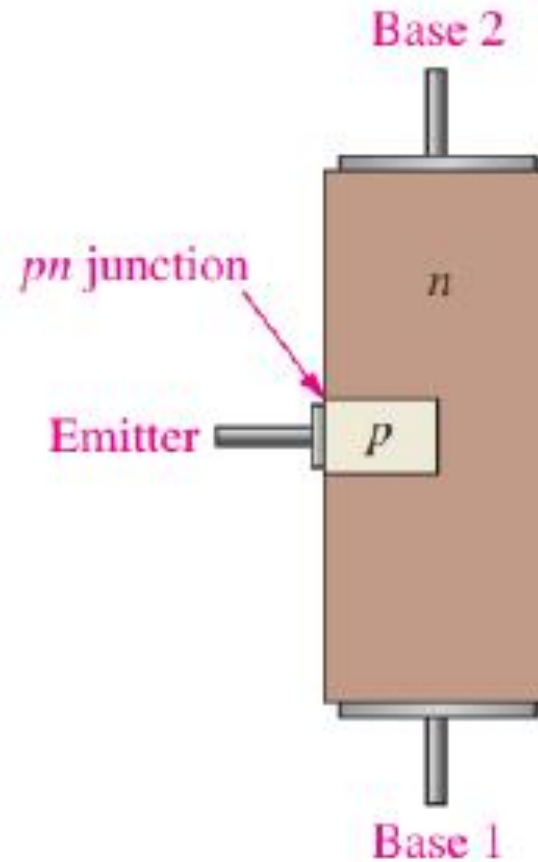

(a) Basic construction

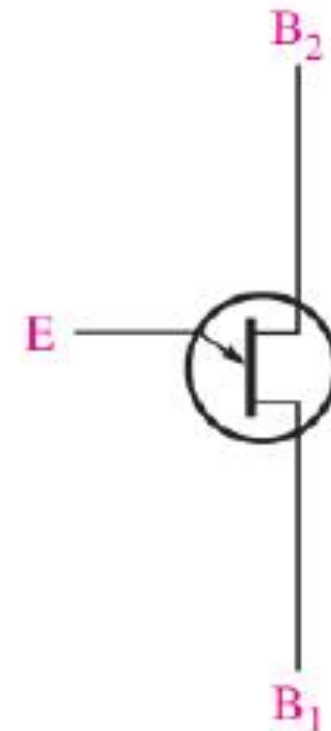

(b) Symbol


UNIJUNCTION TRANSISTOR (UJT)

- Notice the terminals are labelled Emitter (E), Base 1 (B1), and Base 2 (B2).
- Do not confuse this symbol with that of a JFET; the difference is that the arrow is at an angle for the UJT.
- The UJT has only one pn junction, and therefore, the characteristics of this device are different from those of either the BJT or the FET.

Equivalent Circuit

► FIGURE 2-2

UJT equivalent circuit.

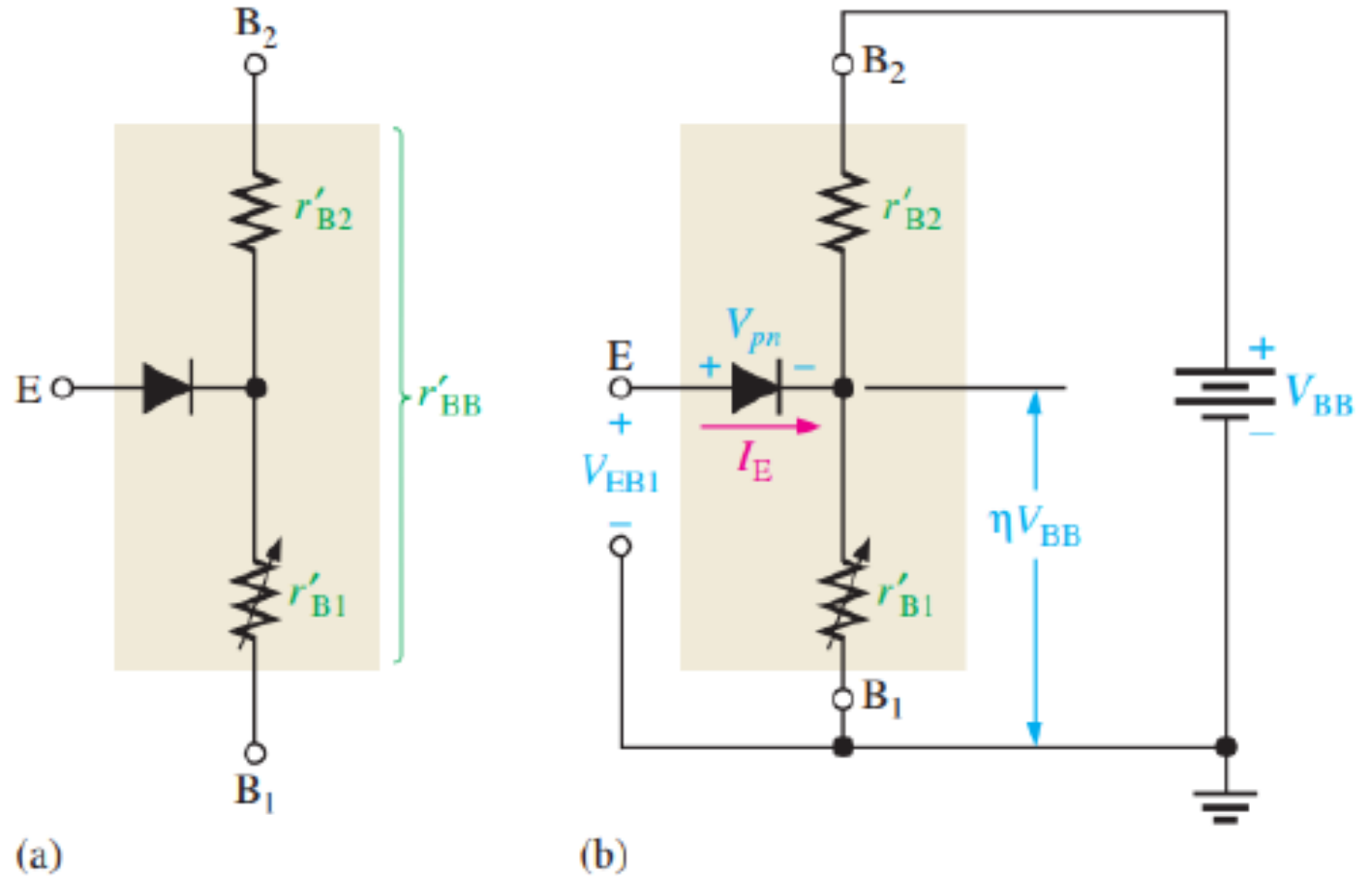

Equivalent Circuit

- The equivalent circuit for the UJT, shown in Figure 2–2(a), will aid in understanding the basic operation.
- The **diode** shown in the figure represents the pn junction r'_{B1} , represents the internal dynamic resistance of the silicon bar between the emitter and base 1, and r'_{B2} represents the dynamic resistance between the emitter and base 2.
- The total resistance between the base terminals is the sum of r'_{B1} and r'_{B2} and is called the interbase resistance, r'_{BB} .

$$r'_{BB} = r'_{B1} + r'_{B2}$$

Equivalent Circuit

- The value of r'_{B1} varies inversely with emitter current I_E , and therefore, it is shown as a variable resistor.
- Depending on I_E , the value of r'_{B1} can vary from several thousand ohms down to tens of ohms.
- The internal resistances r'_{B1} and r'_{B2} form a voltage divider when the device is biased, as shown in Figure 2–2(b).
- The voltage across the resistance r'_{B1} can be expressed as

$$V_{r'_{B1}} = \left(\frac{r'_{B1}}{r'_{BB}} \right) V_{BB}$$

Standoff Ratio (η)


- The ratio $\frac{r'_{B1}}{r'_{BB}}$ is a UJT characteristic called the intrinsic standoff ratio and is designated by “ η ”.

$$\eta = \frac{r'_{B1}}{r'_{BB}}$$

- As long as the applied emitter voltage **V_{EB1} is less than $V_{r'B1} + V_{pn}$** there is no emitter current because the *pn* junction is not forward-biased (V_{pn} is the barrier potential of the *pn* junction).
- The value of emitter voltage that causes the *pn* junction to become forward-biased is called **peak-point voltage** and is expressed as

$$V_P = \eta V_{BB} + V_{pn}$$

- When V_{EB1} reaches V_P , the pn junction becomes forward-biased and I_E begins.
- Holes are injected into the n-type bar from the p-type emitter.
- This increase in holes causes an increase in free electrons, thus increasing the conductivity between emitter and B1 (decreasing r'_{B1}).
- After turn-on, the UJT operates in a negative resistance region up to a certain value of I_E as shown by the characteristic curve in Figure 2–3.

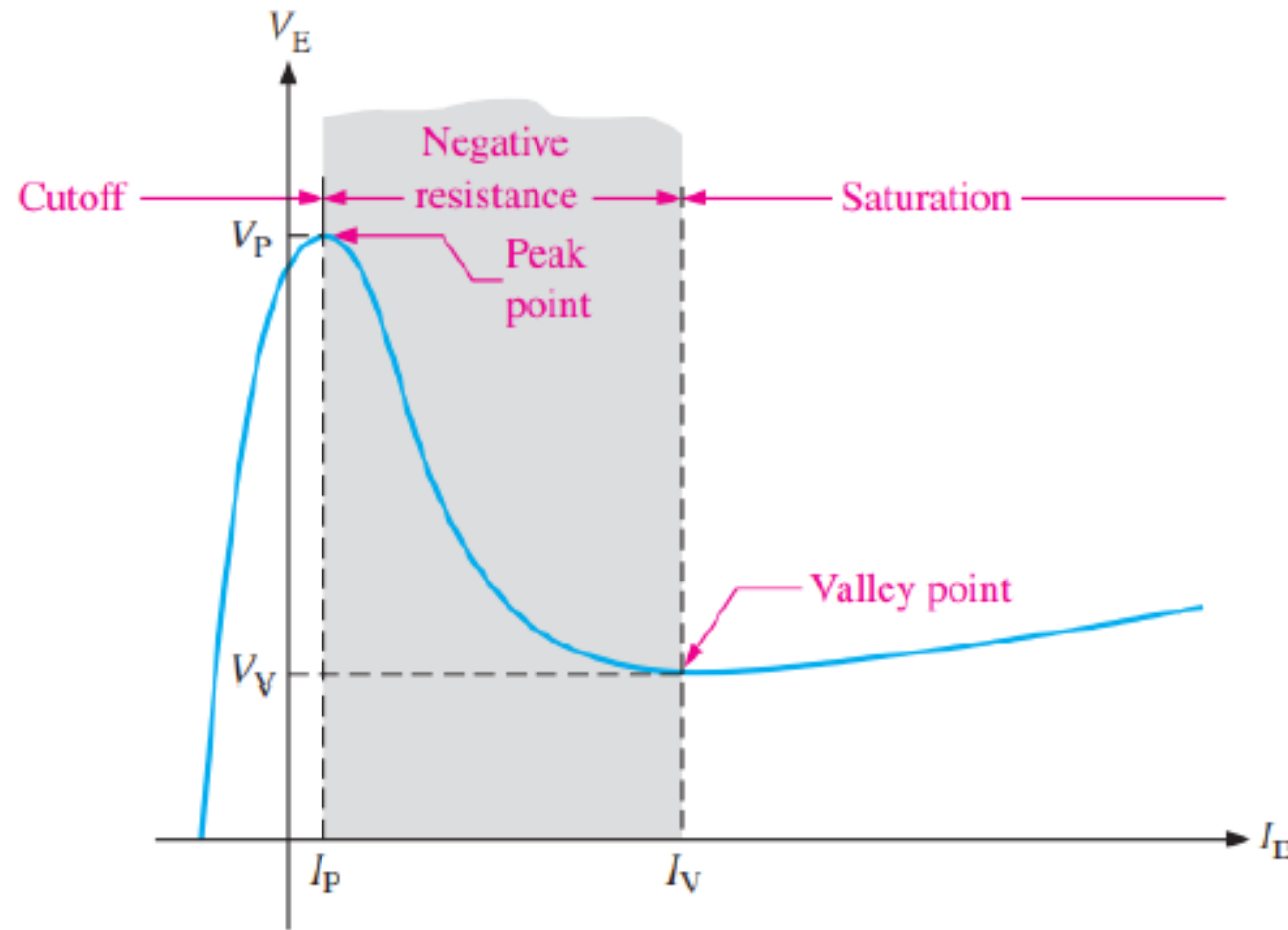


▲ FIGURE 2-3

UJT characteristic curve for a fixed value of V_{BB} .

- As you can see, after the peak point ($V_E = V_P$ and $I_E = I_P$), V_E decreases as I_E continues to increase, thus producing the negative resistance characteristic.
- Beyond the valley point ($V_E = V_V$ and $I_E = I_V$), the device is in saturation, and V_E increases very little with an increasing I_E .

UJT Application

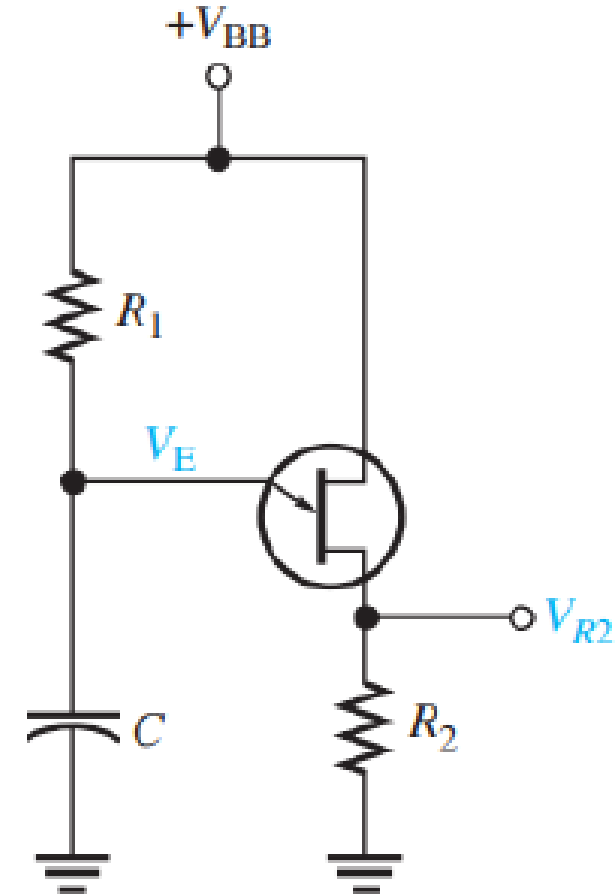- The UJT can be used as a trigger device for SCRs and triacs.
- Other applications include nonsinusoidal oscillators, sawtooth generators, phase control, and timing circuits.
- Figure 2–4 shows a UJT relaxation oscillator as an example of one application.




▲ FIGURE 2-4

Relaxation oscillator.

Relaxation Oscillator

- When dc power is applied, the capacitor C charges exponentially through R1 until it reaches the peak-point voltage VP.
- At this point, the pn junction becomes forward-biased, and the emitter characteristic goes into the negative resistance region (VE decreases and IE increases).
- The capacitor then quickly discharges through the forward-biased junction, r'B, and R2.
- When the capacitor voltage decreases to the valley-point voltage Vv, the UJT turns off, the capacitor begins to charge again, and the cycle is repeated, as shown in the emitter voltage waveform in Figure 2–4 (top).
- During the discharge time of the capacitor, the UJT is conducting. Therefore, a voltage is developed across R2, as shown in the waveform diagram in Figure 2–4 (bottom).
- When a UJT is used as a relaxation oscillator, the **time required** for the capacitor to reach **Vp** is
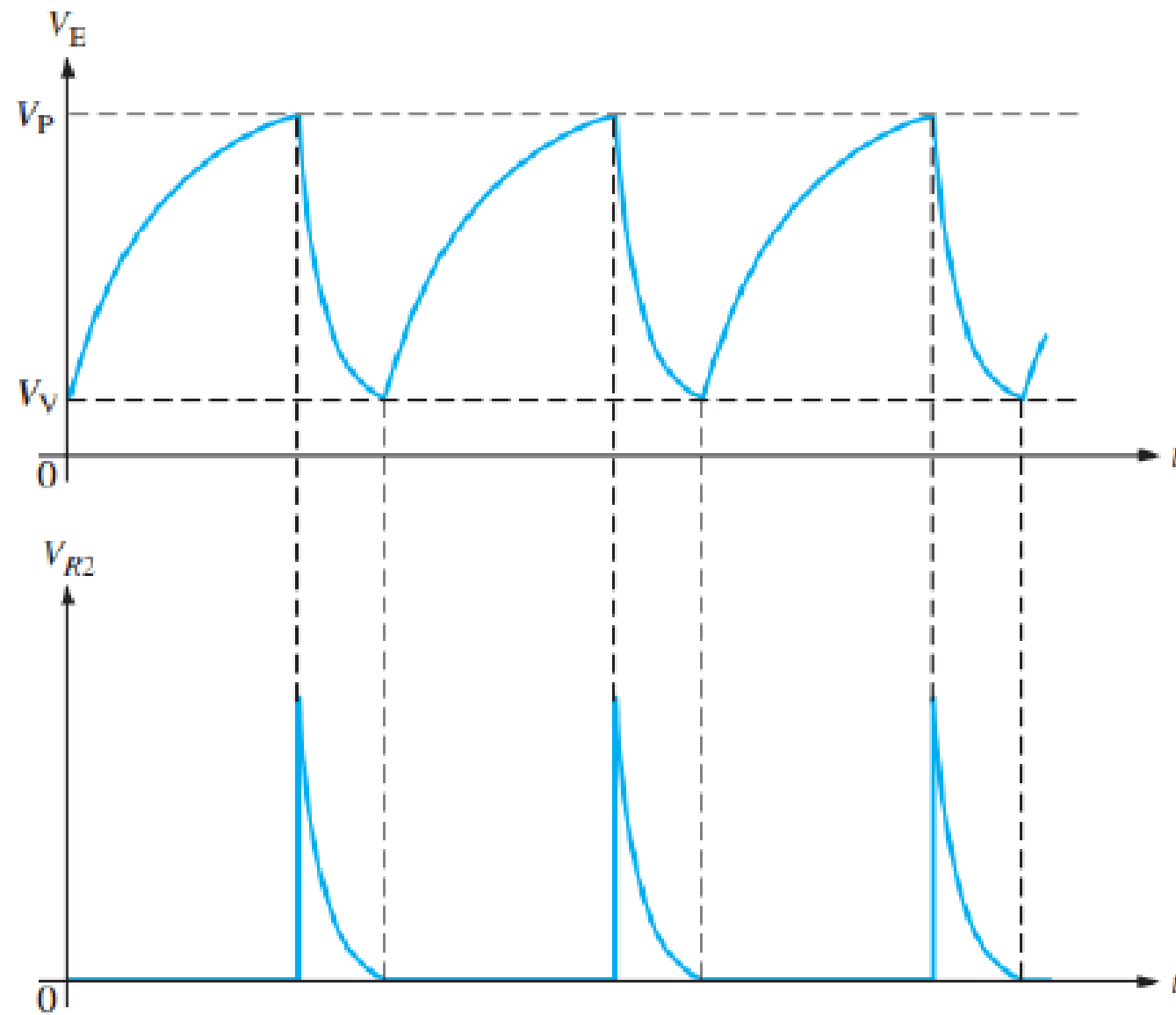
$$T = R_1 C \ln\left(\frac{1}{1-\eta}\right)$$



▲ FIGURE 2-5

Waveforms for UJT relaxation oscillator.

Conditions for Turn-On and Turn-Off

- In the relaxation oscillator of Figure 2–4, certain conditions must be met for the UJT to reliably turn on and turn off.
- First, to ensure turn-on, **R1 must not limit IE at the peak point to less than IP.**
- To ensure this, the voltage drop across R1 at the peak point should be greater than $I_P R_1$. Thus, the condition for turn-on is

$$V_{BB} - V_P > I_P R_1$$

or

$$R_1 < \frac{V_{BB} - V_P}{I_P}$$

- To ensure turn-off of the UJT at the valley point, R_1 must be large enough that I_E (at the valley point) can decrease below the specified value of I_V .
- This means that the voltage across R_1 at the valley point must be less than $I_V R_1$. Thus, the condition for turn-off is

$$V_{BB} - V_V < I_V R_1$$

or

$$R_1 > \frac{V_{BB} - V_V}{I_V}$$

- Therefore, for a proper turn-on and turn-off, R must be in the range

$$\frac{V_{BB} - V_P}{I_P} > R_1 > \frac{V_{BB} - V_V}{I_V}$$

Programmable Unijunction Transistor(PUT)


Programmable Unijunction Transistor(PUT)

- Programmable unijunction transistor or PUT is a close relative of the thyristor family.
- Its has a four layered construction just like the thyristors and have three terminals named anode(A), cathode(K) and gate(G) again like the thyristors.
- Some call it a programmable UJT just because its characteristics and parameters have much *similarity* to that of the *unijunction transistor*.
- It is called programmable because the parameters like intrinsic **standoff ratio** (η), **peak voltage**(V_p), etc. can be programmed with the help of two external resistors.
- The main application of programmable UJT are relaxation oscillators , thyristor firing, pulse circuits and timing circuits.


Programmable Unijunction Transistor(PUT)

► FIGURE 2-6

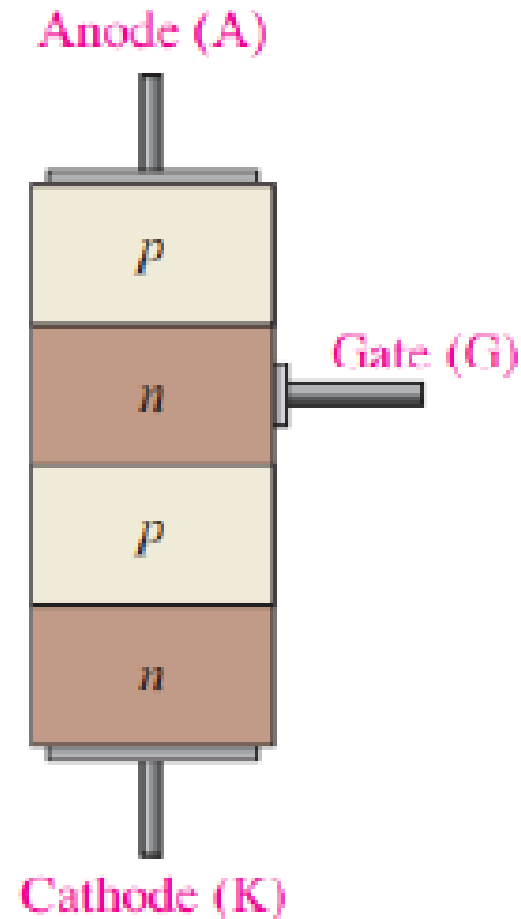The programmable unijunction transistor (PUT).



(a) Basic construction

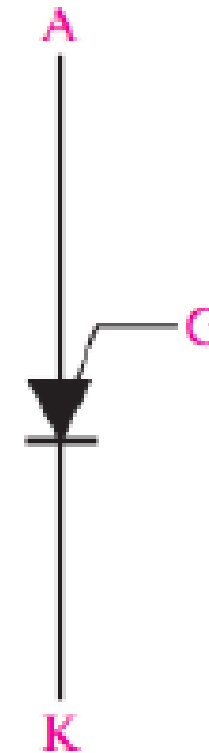

(b) Symbol

PUT characteristics

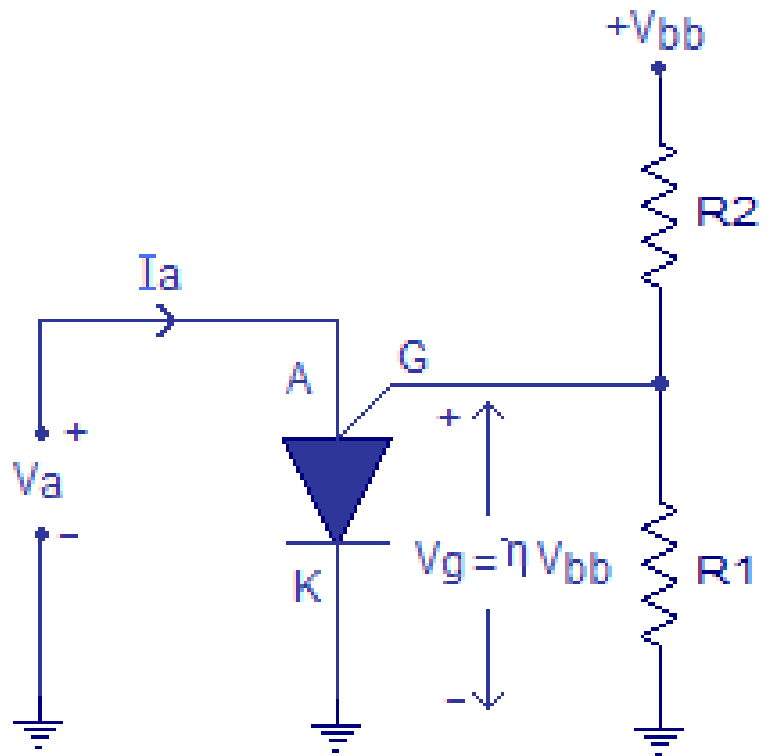


Fig 3: PUT biasing circuit

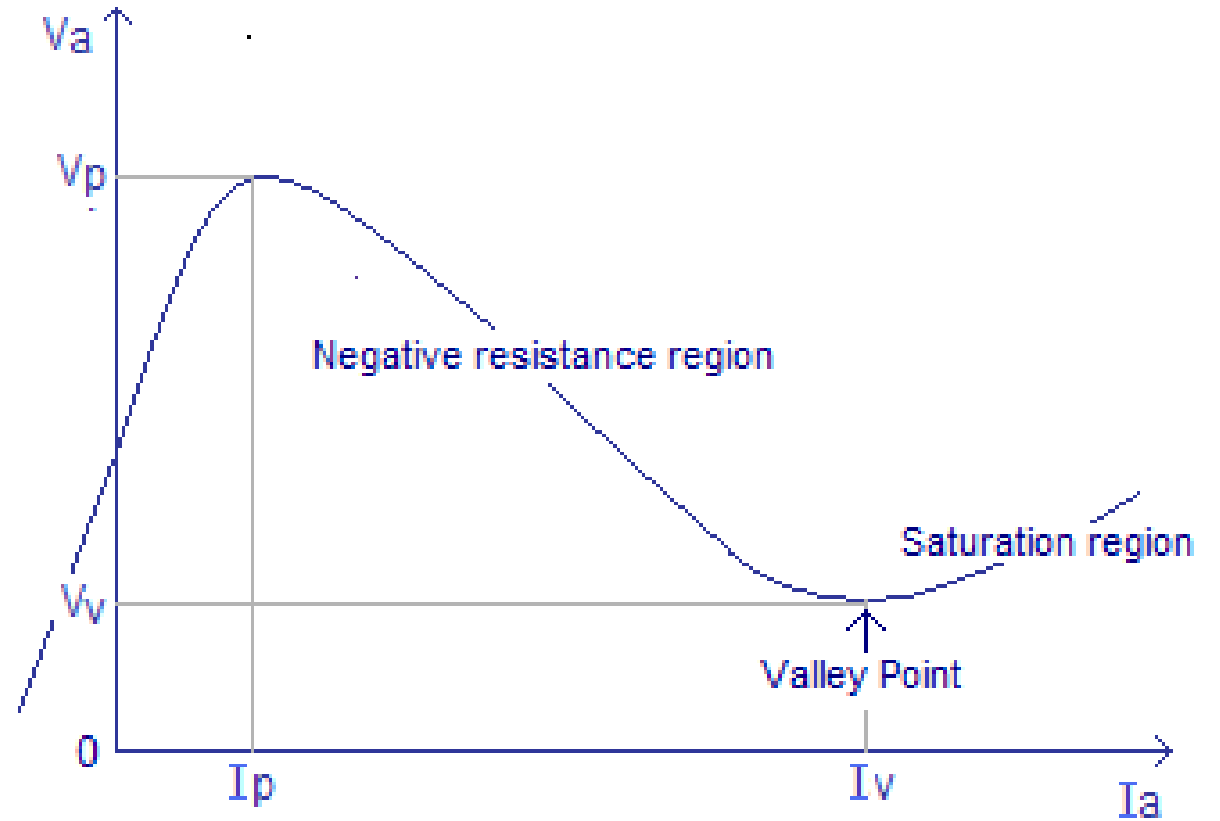


Fig 4: PUT characteristics

PUT Operation

- Typically the anode of the PUT is connected to a positive voltage and the cathode is connected to the ground.
- The gate is connected to the junction of the two external resistor R_1 and R_2 which forms a voltage divider network. It is the value of these two resistors that determines the intrinsic standoff ratio(η) and peak voltage (V_p) of the PUT.
- When the anode to cathode voltage (V_a) is increased the anode current will also get increased and the junction behaves like a typical P-N junction. But the V_a cannot be increased beyond a particular point.
- At this point sufficient number of charges are injected and the junction starts to saturate. Beyond this point the anode current (I_a) increases and the anode voltage (V_a) decreases.

PUT Operation

- This is equal to a negative resistance scenario and this negative resistance region in the PUT characteristic is used in relaxation oscillators.
- When the anode voltage (V_a) is reduced to a particular level called “Valley Point”, the device becomes fully saturated and no more decrease in V_a is possible. There after the device behaves like a fully saturated P-N junction.

Peak Voltage (V_p)

- It is the anode to cathode voltage after which the PUT jumps into the negative resistance region.
- The peak voltage V_p will be usually one diode drop (0.7V) plus the gate to cathode voltage (V_g).
- Peak voltage can be expressed using the equation:


$$V_P = 0.7 \text{ V} + V_G = 0.7 \text{ V} + V_{R1} = 0.7 \text{ V} + \eta V_{BB}$$

Programmable Unijunction Transistor(PUT)

- Notice that the gate is connected to the **n region** adjacent to the anode.
- This pn junction controls the on and off states of the device.
- The gate is always biased positive with respect to the cathode.
- When the anode voltage exceeds the gate voltage by approximately 0.7 V, the pn junction is forward-biased and the PUT turns on.
- The PUT stays on until the anode voltage falls back below this level, then the PUT turns off.

Setting the Trigger Voltage

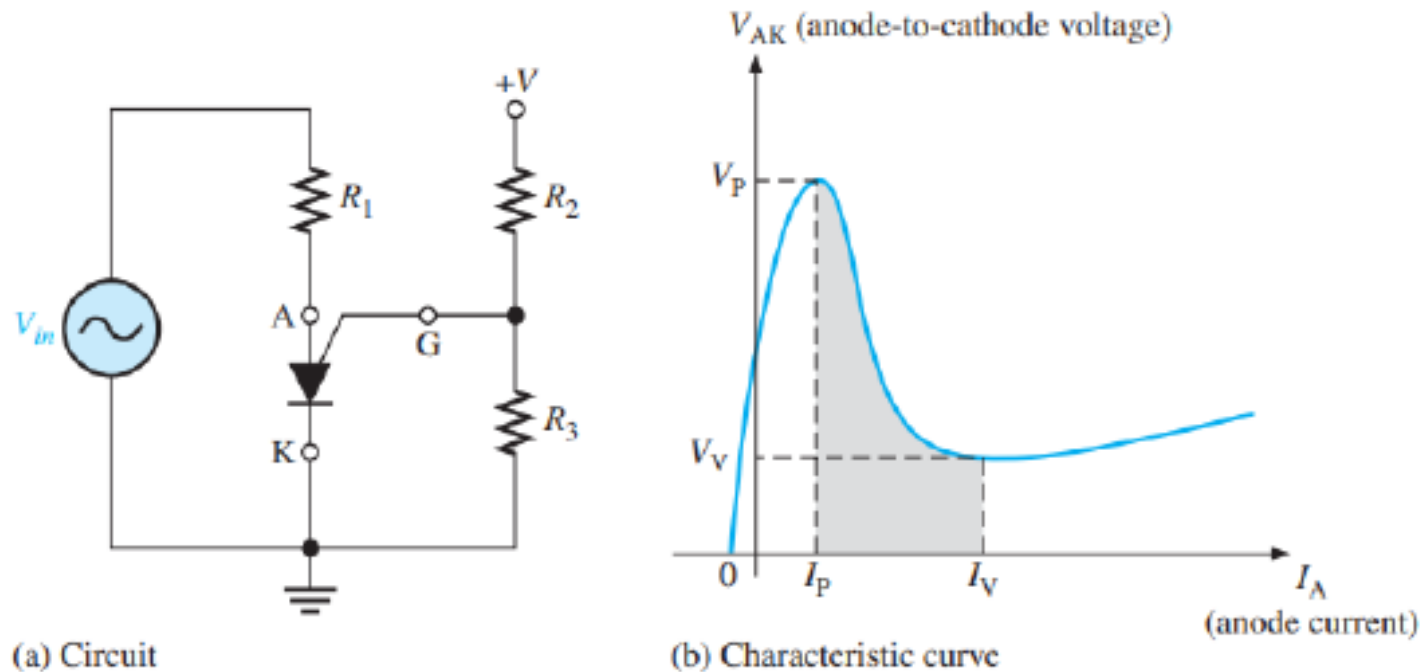- The gate can be biased to a desired voltage with an external voltage divider, as shown in Figure 2–7(a), so that when the anode voltage exceeds this “programmed” level, the PUT turns on




▲ FIGURE 2-7


PUT biasing.

Application of PUT

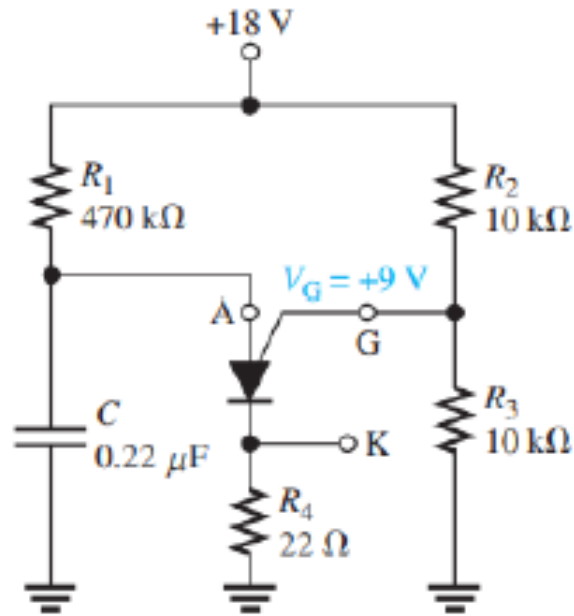- A plot of the anode-to-cathode voltage, V_{AK} , versus anode current, I_A , in Figure 2–7 (b) reveals a characteristic curve similar to that of the UJT. Therefore, the PUT replaces the UJT in many applications. One such application is the relaxation oscillator in Figure 2–8 (a).



(a)

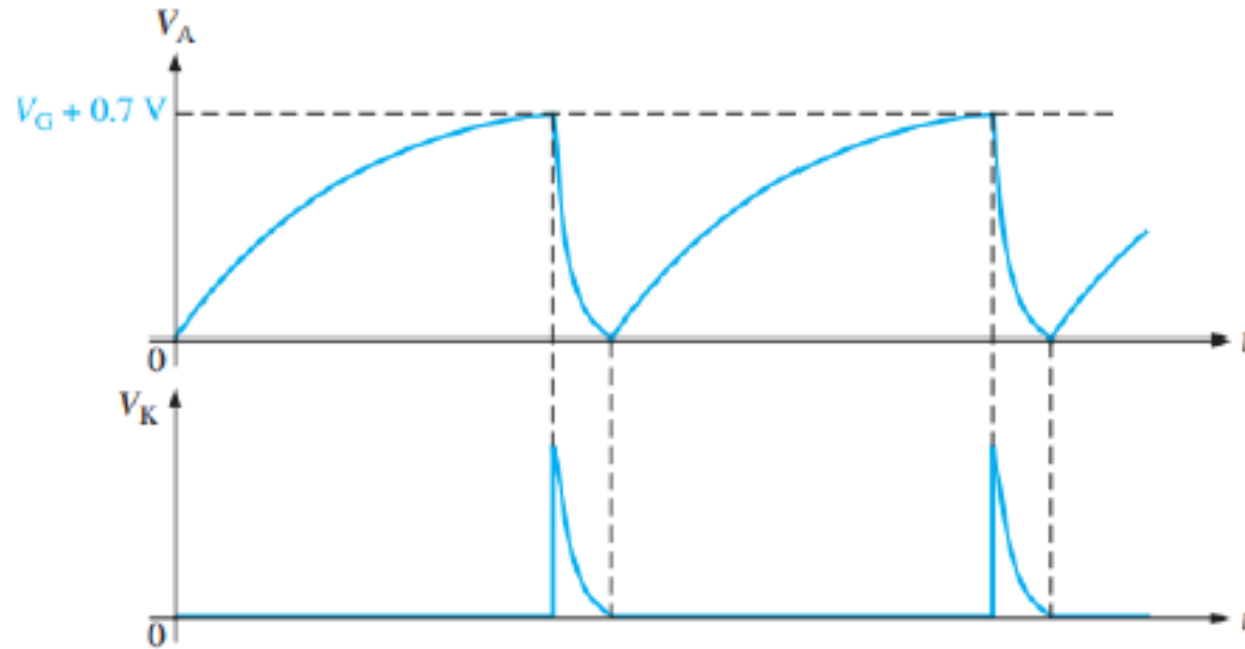

(b)

▲ FIGURE 2-8

PUT relaxation oscillator.

The basic operation of the PUT is as follows:

- The gate is biased at +9 V by the voltage divider consisting of resistors R2 and R3.
- When dc power is applied, the PUT is off and the capacitor charges toward +18 V through R1.
- When the capacitor reaches $V_G + 0.7$ V, the PUT turns on and the capacitor rapidly discharges through the low on resistance of the PUT and R4.
- A voltage spike is developed across R4 during the discharge.
- As soon as the capacitor discharges, the PUT turns off and the charging cycle starts over, as shown by the waveforms in Figure 2–8(b).

Sample Problems

Problem #1

- The datasheet of a certain UJT gives $\eta = 0.6$. Determine the peak-point emitter voltage V_P if $V_{BB} = 20\text{ V}$.

Ans.

$$V_P = 12.7\text{ V}$$

Problem #2

- Determine a value of R_1 in Figure 2-9 that will ensure proper turn-on and turn-off of the UJT. The characteristic of the UJT exhibits the following values: $\eta = 0.5$, $V_V = 1$ V, $I_V = 10$ mA, $I_P = 20$ μ A, and $V_P = 14$ V.

Ans.

$$800 \text{ k}\Omega > R_1 > 2.9 \text{ k}\Omega$$

Problem #3

In Figure 2-9, $C_T = 0.1 \mu\text{F}$ and $R_T = 220 \text{ k}\Omega$.

- Calculate the frequency of the emitter voltage waveform.

Assume $\eta = 0.6$.

Ans.

$$f = 49.6 \text{ Hz}$$

► FIGURE 2-9

