

RELAXATION OSCILLATORS

RELAXATION OSCILLATORS



- Relaxation oscillators use an RC timing circuit and a device that changes states to generate a periodic waveform.

Common Relaxation Oscillators:

- **Triangular-Wave Oscillator**
- **Practical Triangular-Wave Oscillator**
- **Sawtooth Voltage-Controlled Oscillator (VCO)**
- **Square-Wave Oscillator**
- **555 TIMER as an Oscillator**

Triangular-Wave Oscillator

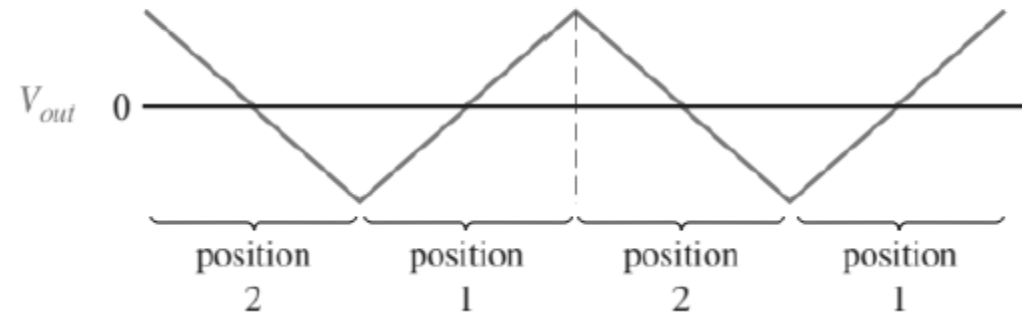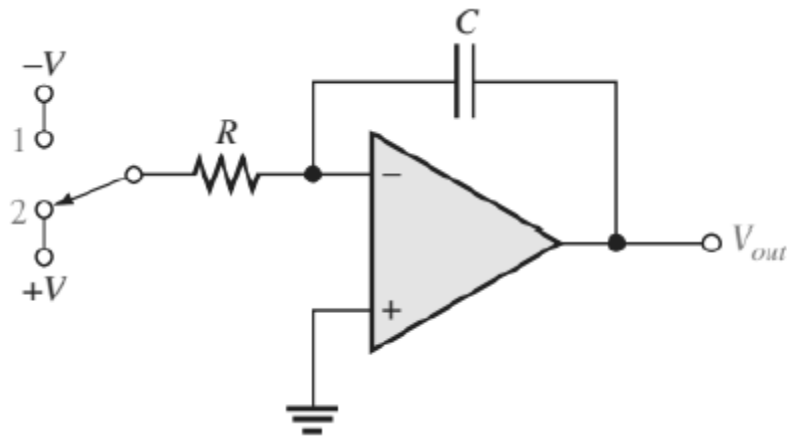
- The **op-amp integrator** can be used as the basis for a triangular-wave oscillator.



- When the switch is in position 1, the negative voltage is applied, and the output is a positive-going ramp.
- When the switch is thrown into position 2, a negative-going ramp is produced.
- If the switch is thrown back and forth at fixed intervals, the output is a triangular wave consisting of alternating positive-going and negative-going ramps.



Practical Triangular-Wave Oscillator

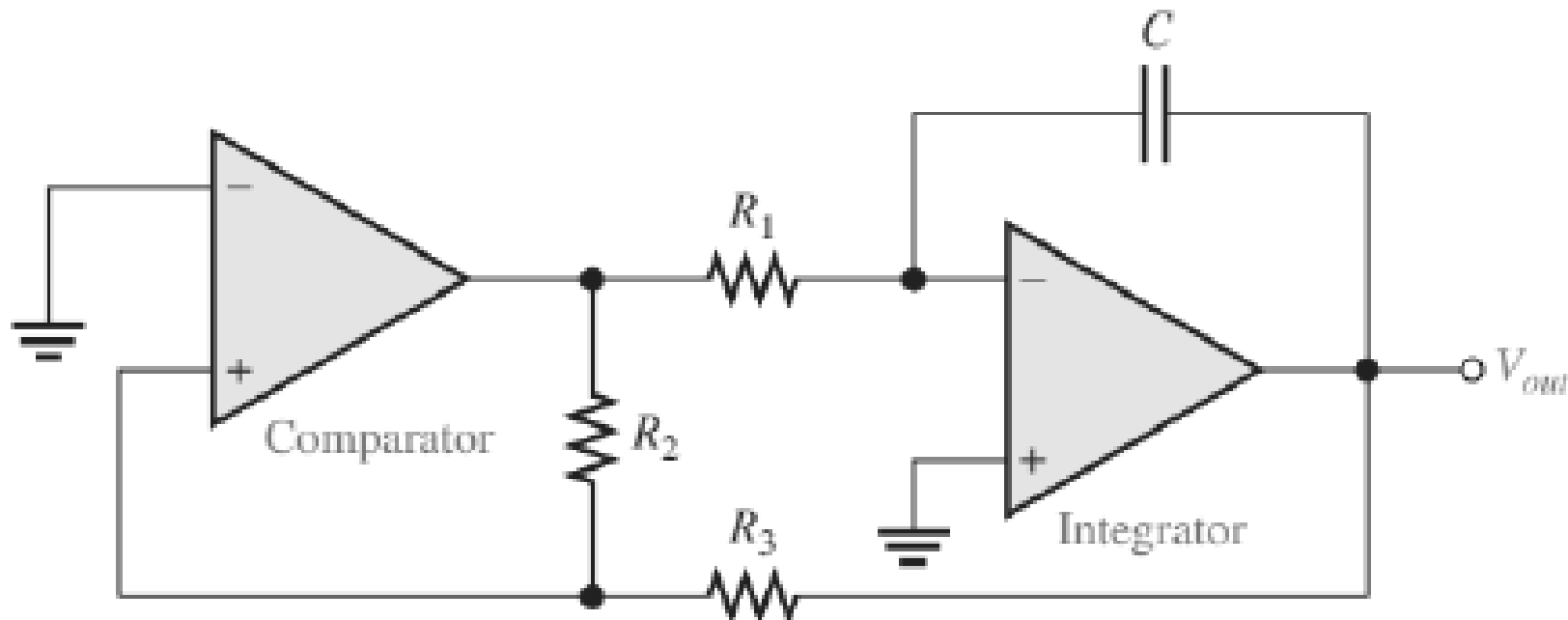- One practical implementation of a triangular-wave oscillator utilizes an op-amp comparator with **hysteresis** to perform the switching function, as shown in Figure below.





Practical Triangular-Wave Oscillator

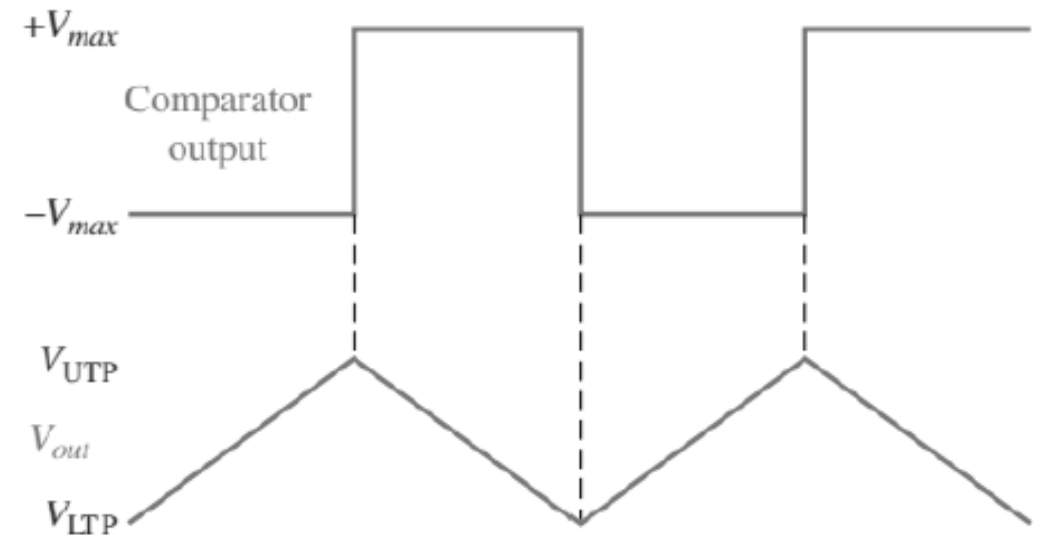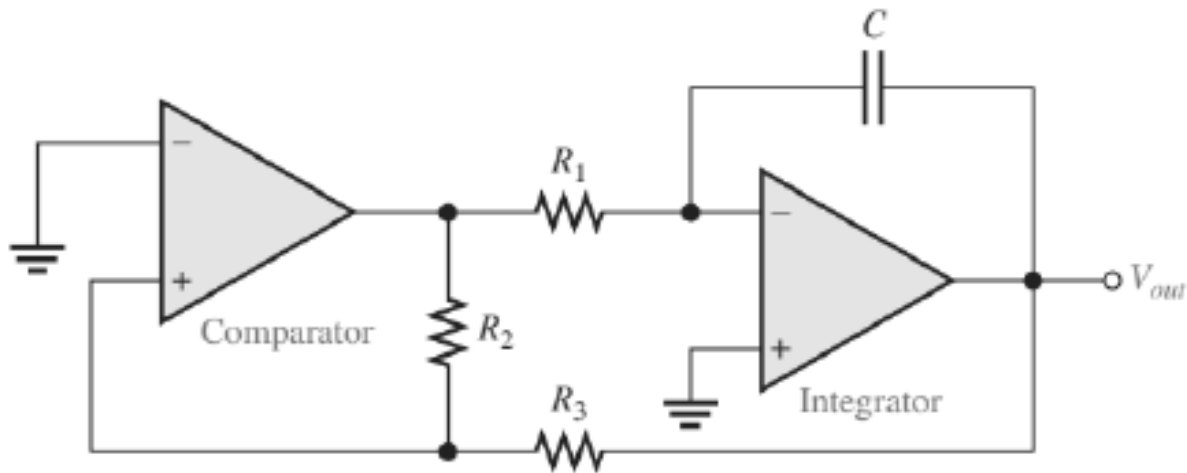- To begin, assume that the output voltage of the comparator is at its maximum negative level. This output is connected to the inverting input of the integrator through R_1 , producing a positive-going ramp on the output of the integrator.



Practical Triangular-Wave Oscillator

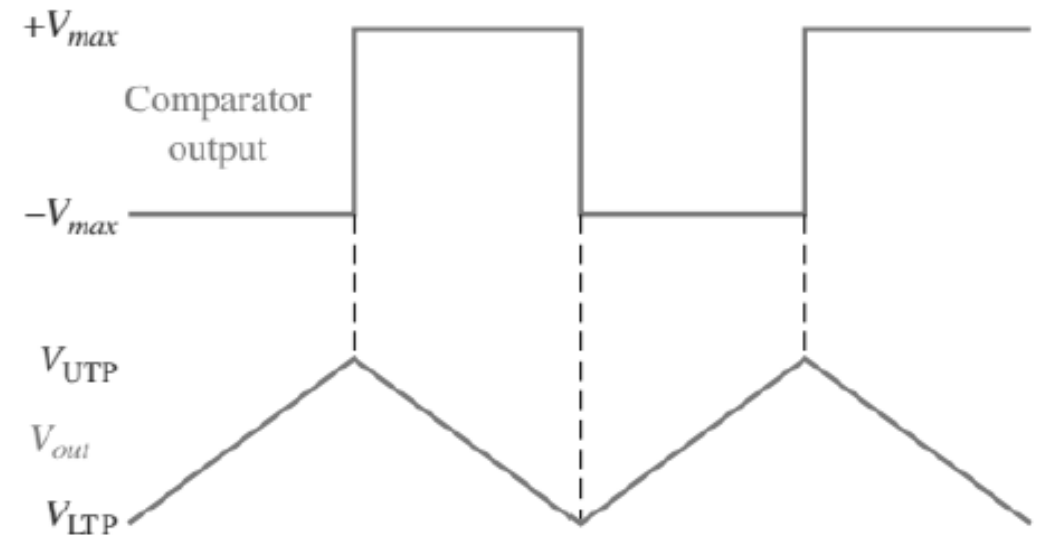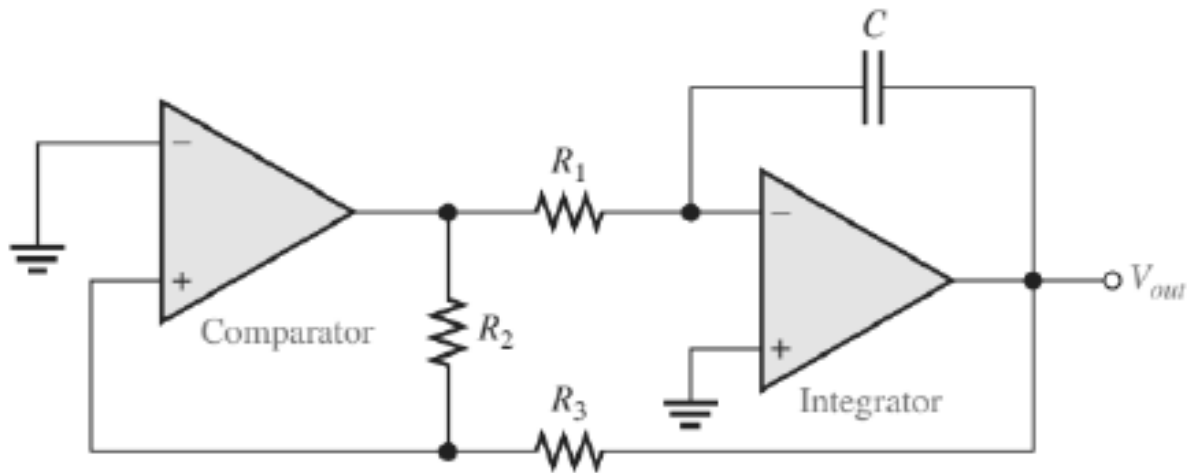- When the ramp voltage reaches the **upper trigger point (UTP)**, the comparator switches to its maximum positive level. This positive level causes the integrator ramp to **change to a negative-going** direction.
- The ramp continues in this direction until the **lower trigger point (LTP)** of the comparator is reached.



Practical Triangular-Wave Oscillator

- Since the comparator produces a square-wave output, the circuit can be used as both a **triangular-wave oscillator** and a **square-wave oscillator**.
- Devices of this type are commonly known as **function**
- **generators** because they produce **more than one output function**.
- The output amplitude of the **square wave** is set by the **output swing of the comparator**, and the resistors **R_2 and R_3** set the amplitude of the **triangular output** by establishing the UTP and LTP voltages.

Practical Triangular-Wave Oscillator

- Upper Trigger Point Voltage (V_{UTP}):

$$V_{UTP} = +V_{\max} \frac{R_3}{R_2}$$

- Lower Trigger Point Voltage (V_{LTP}):

$$V_{LTP} = -V_{\max} \frac{R_3}{R_2}$$

- Frequency of both waveforms:


$$f_r = \frac{1}{4R_1C} \left(\frac{R_2}{R_3} \right)$$

Frequency depends on the R_1C time constant as well as the amplitude-setting resistors, R_2 and R_3 .
By varying R_1 , the frequency of oscillation can be adjusted **without changing the output amplitude**.


Sawtooth Voltage-Controlled Oscillator (VCO)

- The **voltage-controlled oscillator (VCO)** is a relaxation oscillator whose frequency can be changed by a **variable dc control voltage**.
- VCOs can be either **sinusoidal or nonsinusoidal**.
- One way to build a sawtooth VCO is with an **op-amp integrator** that uses a switching device (**PUT**) in parallel with the feedback capacitor to **terminate each ramp** at a prescribed level and effectively “reset” the circuit.

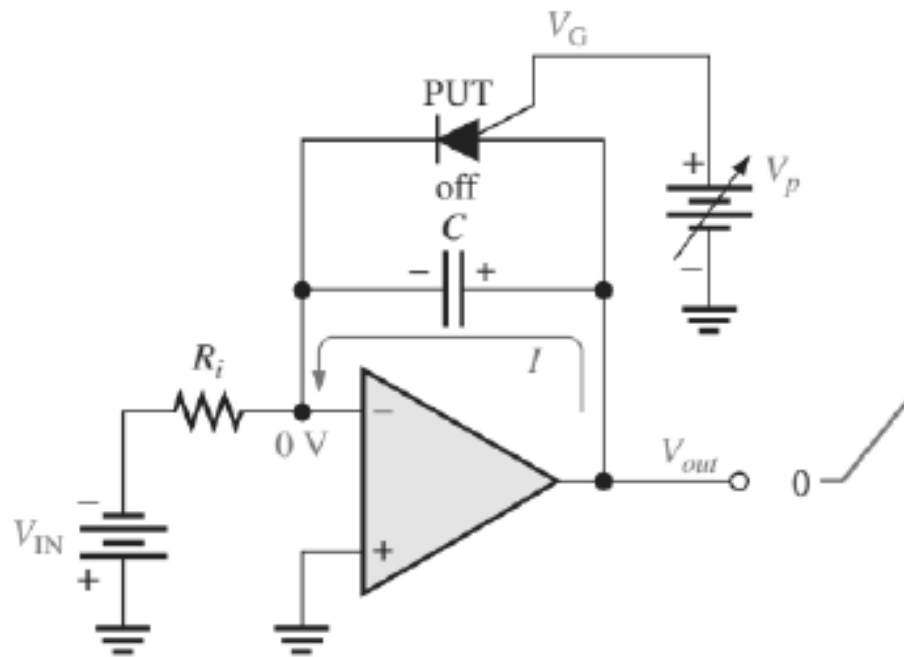Sawtooth Voltage-Controlled Oscillator (VCO)



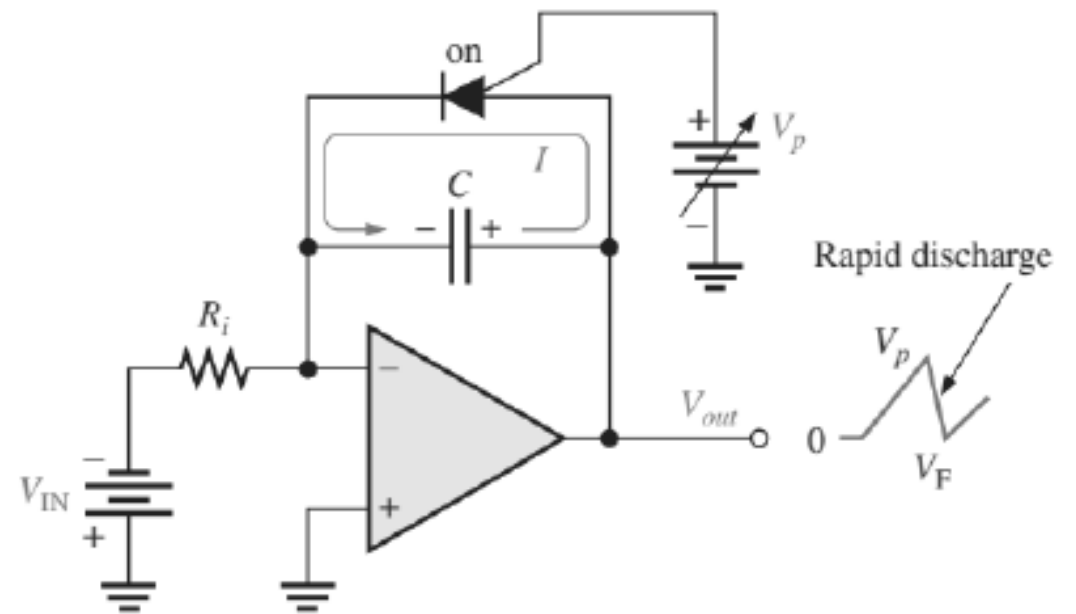(a) Initially, the capacitor charges, the output ramp begins, and the PUT is off.



(b) The capacitor rapidly discharges when the PUT momentarily turns on.

Sawtooth Voltage-Controlled Oscillator (VCO)

- As you learned in Module number 2, the PUT is a programmable unijunction transistor with an anode, a cathode, and a gate terminal.
- The gate is always biased positively with respect to the cathode.
- When the anode voltage exceeds the gate voltage by approximately 0.7 V, the PUT turns on and acts as a forward-biased diode.
- When the anode voltage falls below this level, the PUT turns off.
- Also, the current must be above the holding value to maintain conduction.
- The operation of the sawtooth VCO begins when the negative dc input voltage, $-V_{IN}$ produces a positive going ramp on the output.

Sawtooth Voltage-Controlled Oscillator (VCO)

- During the time that the **ramp is increasing**, the circuit acts as a **regular integrator**.
- The PUT triggers on when the output ramp (at the anode) exceeds the gate voltage by 0.7 V. The gate is set to the approximate desired sawtooth peak voltage.
- When the PUT turns on, the capacitor rapidly discharges, as shown in Figure (b).
- The capacitor does not discharge completely to zero because of the PUT's forward voltage, V_F .
- Discharge continues until the PUT current falls below the holding value. At this point, the PUT turns off and the capacitor begins to charge again, thus generating a new output ramp. The cycle continually repeats, and the resulting output is a repetitive sawtooth waveform.
- The sawtooth amplitude and period can be adjusted by varying the PUT **gate voltage**.

Sawtooth Voltage-Controlled Oscillator (VCO)

Period (T) and Frequency of oscillation (f_r):

- The time it takes a capacitor to charge from V_F to V_P is the period, T, of the sawtooth waveform (neglecting the rapid discharge time).



$$T = \frac{V_P - V_F}{|V_{in}|/R_i C}$$

- Frequency of Oscillation:

$$f = 1/T = \frac{|V_{in}|}{R_i C} \left(\frac{1}{V_P - V_F} \right)$$

Square-Wave Oscillator

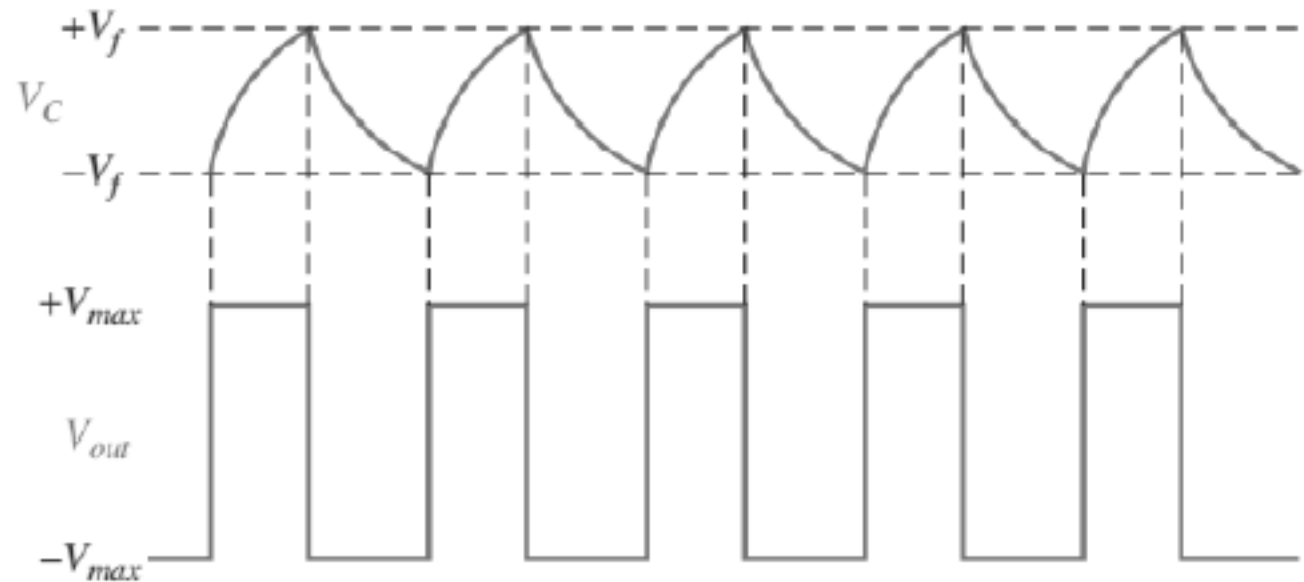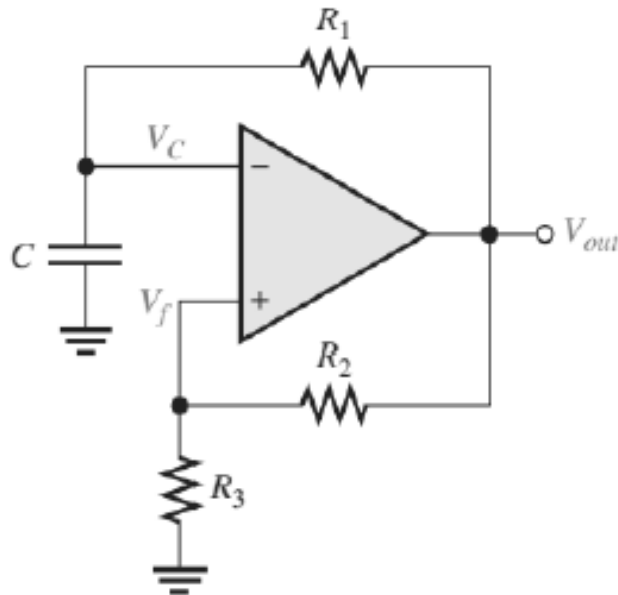- The basic square-wave oscillator shown in Figure is a type of relaxation oscillator because its operation is based on the charging and discharging of a capacitor.
- Notice that the op-amp's inverting input is the capacitor voltage and the noninverting input is a portion of the output fed back through resistors R_2 and R_3 to provide hysteresis.




Square-Wave Oscillator

- When the circuit is first turned on, the capacitor is **uncharged**, and thus the **inverting input is at 0 V**. This makes the output a **positive maximum**, and the capacitor begins to charge toward V_{out} through $R1$.
- When the capacitor voltage (V_C) reaches a value equal to the feedback voltage (V_f) on the noninverting input, the **op-amp switches to the maximum negative state**.
- At this point, the capacitor begins to discharge from $+V_f$ toward $-V_f$.
- When the capacitor voltage reaches $-V_f$, the op-amp switches back to the maximum positive state. This action continues to repeat, as shown in the Figure and a square-wave output voltage is obtained.


555 TIMER

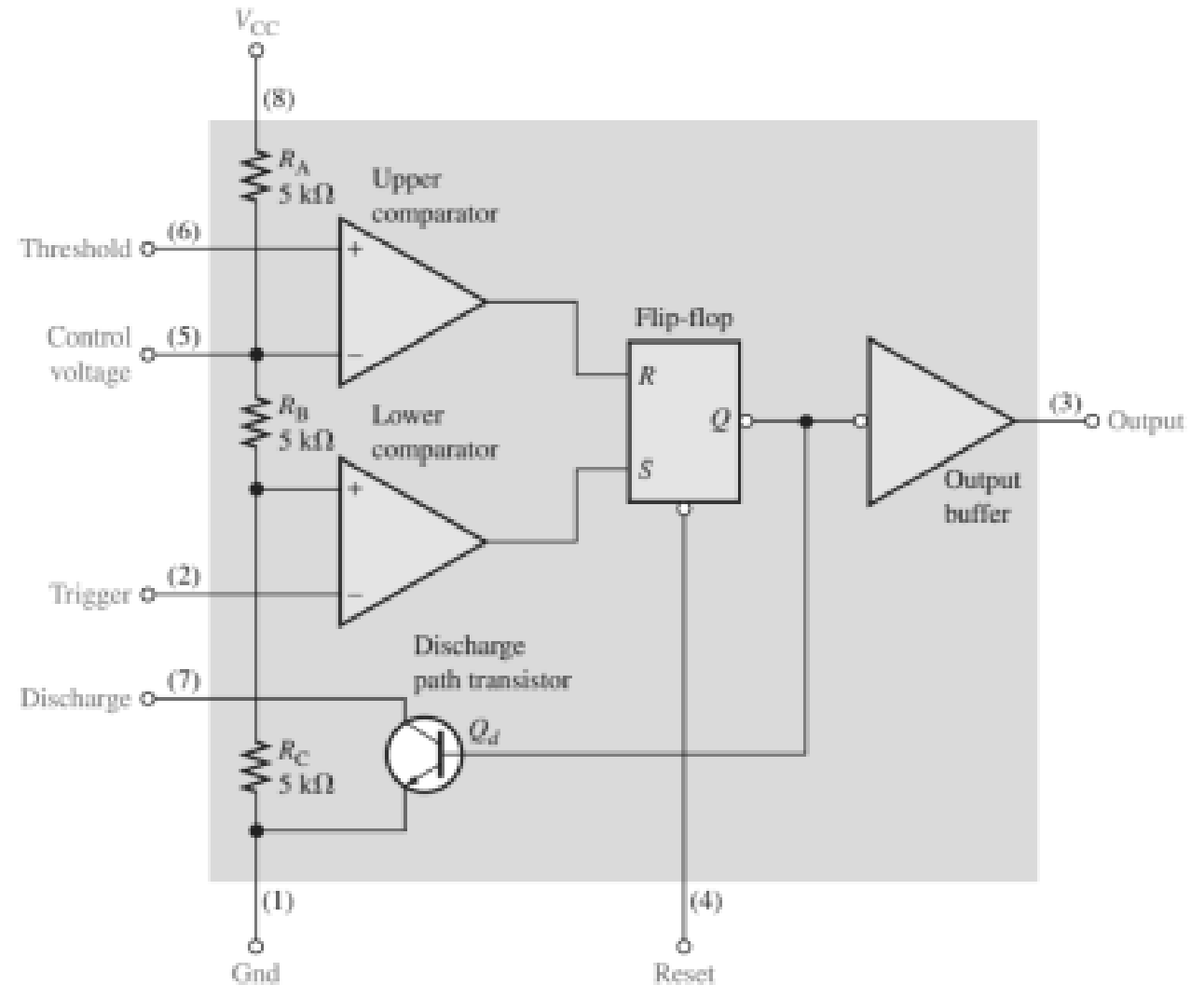- The 555 timer consists basically of **two comparators**, a **flip-flop**, a **discharge transistor**, and a **resistive voltage divider**, as shown in the figure.




555 TIMER

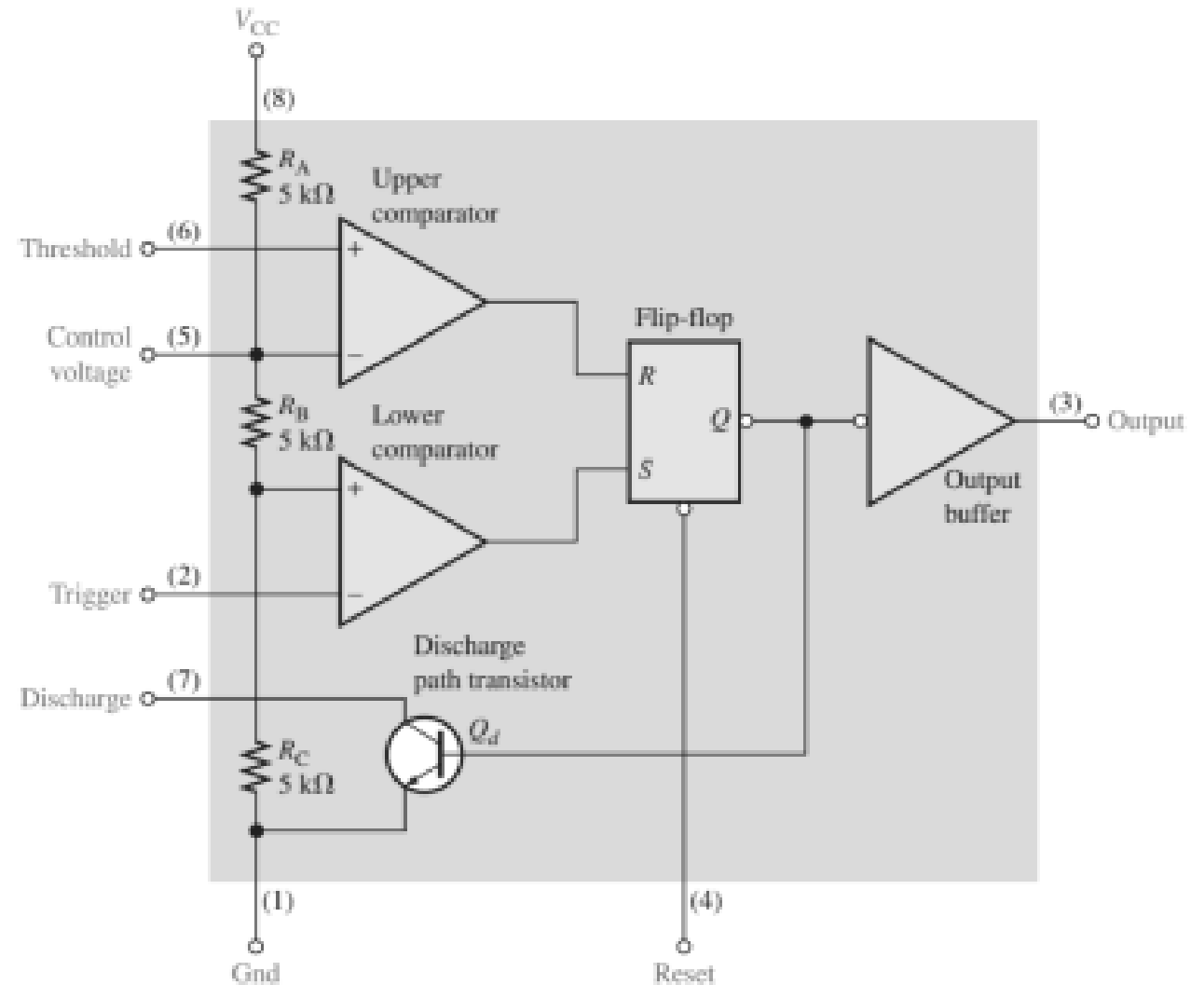- Flip-flop
 - It is a **two-state device** whose output can be at either a high voltage level (set, S) or a low voltage level (reset, R). The state of the output can be changed with proper input signals.




555 TIMER

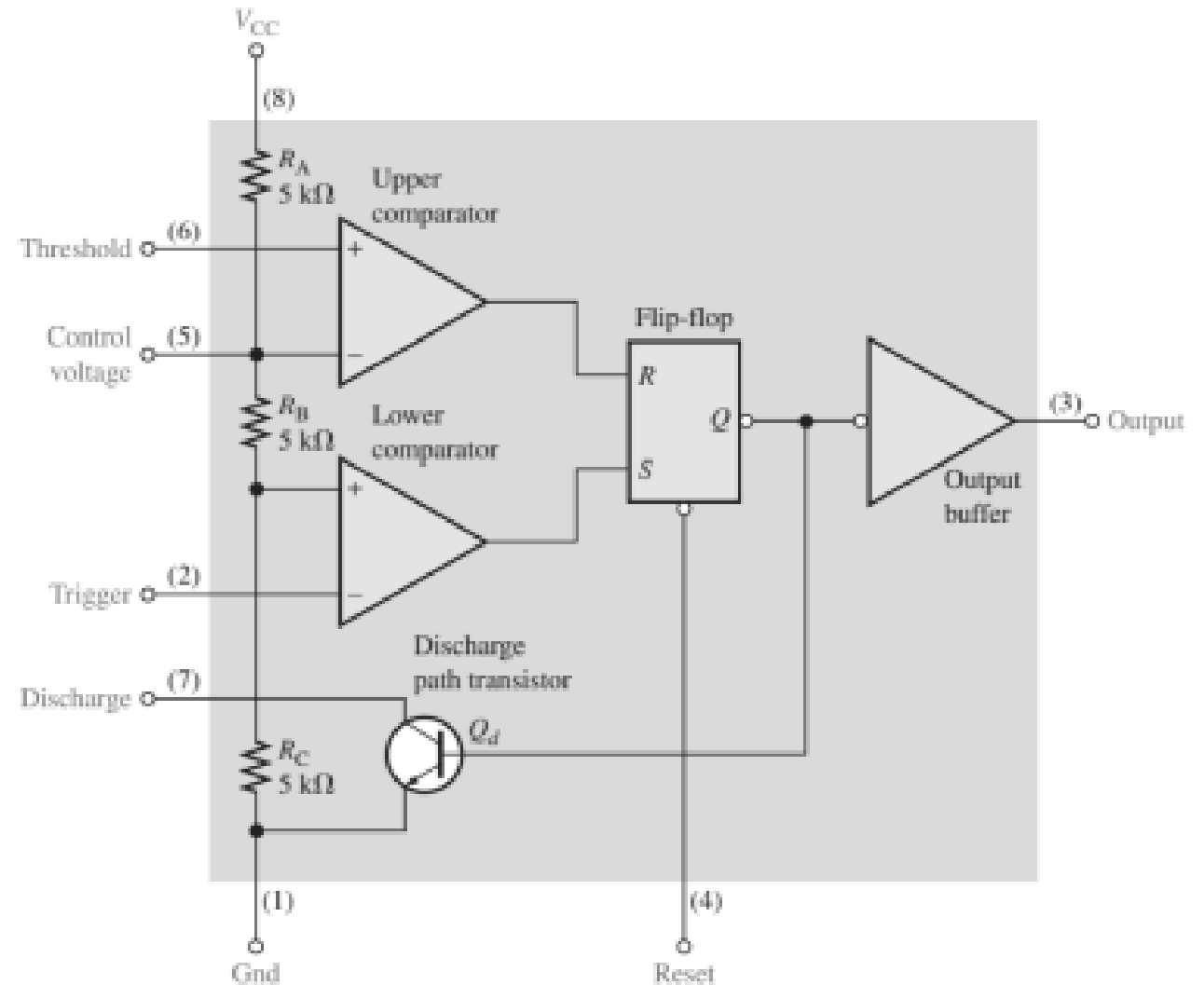- The resistive voltage divider is used to set the voltage comparator levels.
- All three resistors are of equal value; therefore, the upper comparator has a reference of $\frac{2}{3}V_{CC}$, and the lower comparator has a reference of $\frac{1}{3}V_{CC}$.




555 TIMER

- The comparators' outputs control the state of the flip-flop.
- When the trigger voltage goes below $\frac{1}{3}V_{CC}$, the flip-flop sets and the output jumps to its **high level**.
- The threshold input is normally connected to an external RC timing circuit.
- When the external capacitor voltage exceeds $\frac{2}{3}V_{CC}$, the upper comparator resets the flip-flop, which in turn switches the output back to its **low level**.

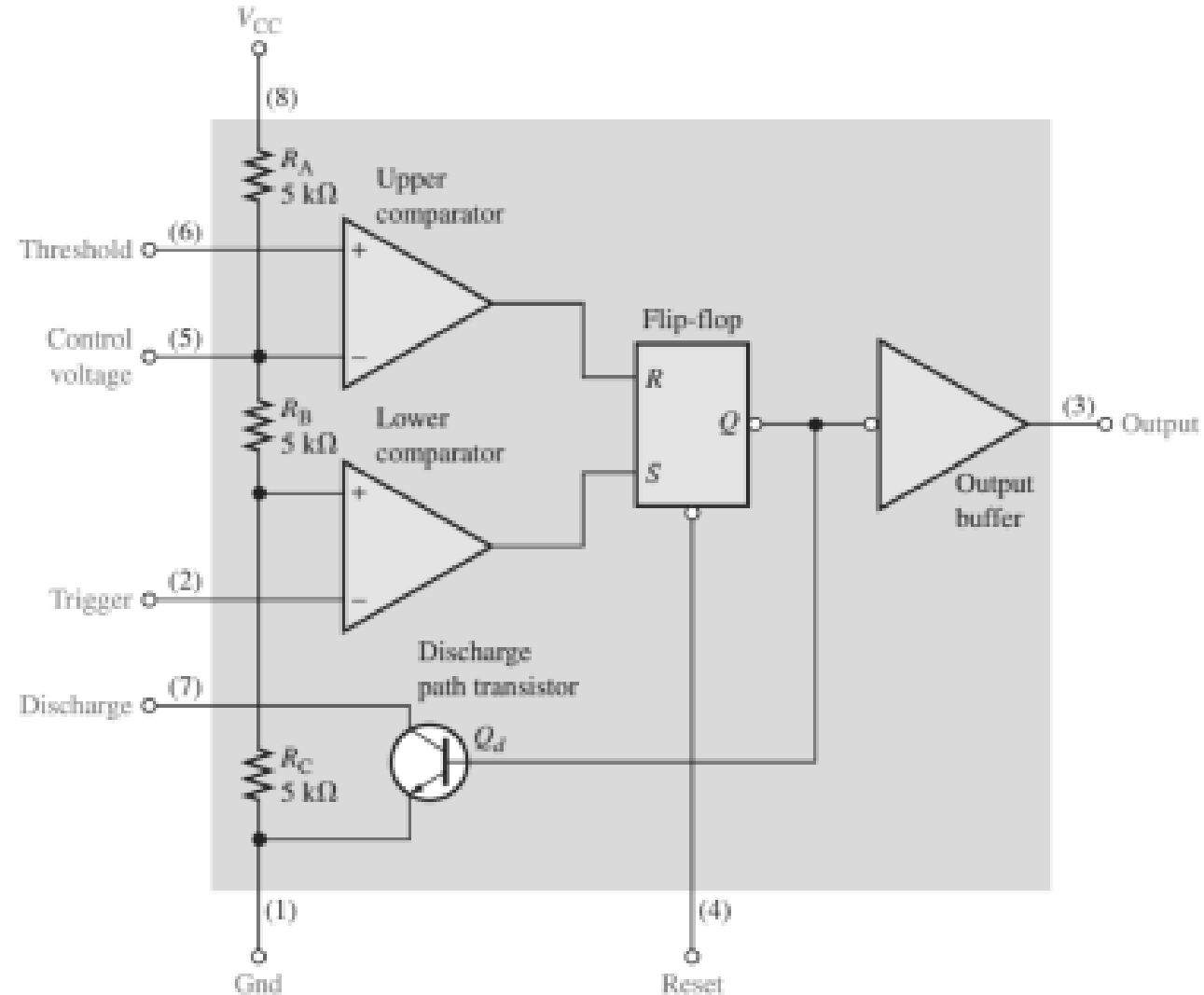


555 TIMER

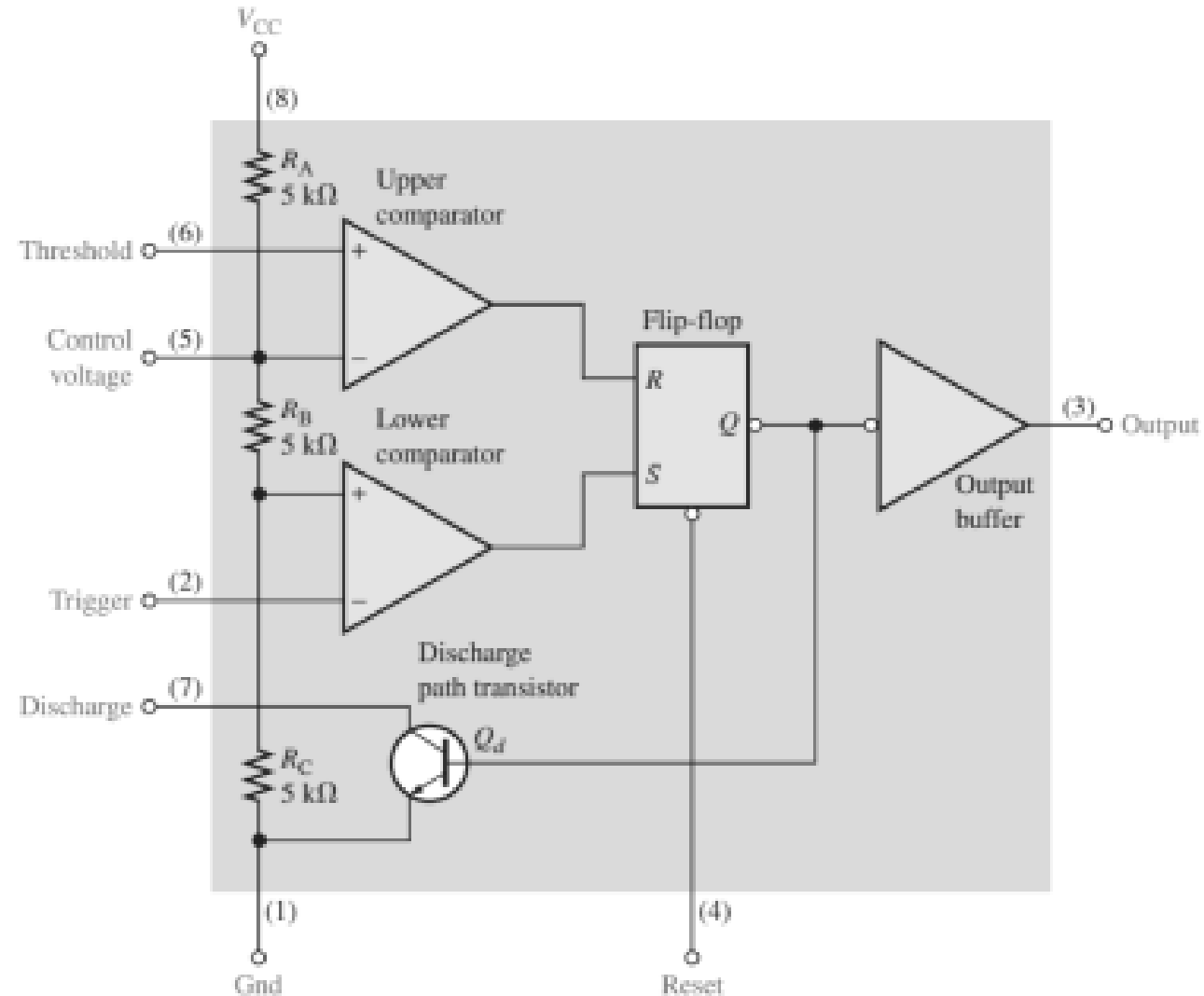- When the device output is low, the **discharge transistor (Q_d)** is turned on and provides a path for rapid discharge of the external timing capacitor.
- This basic operation allows the timer to be configured with external components as an **oscillator**, a **one-shot**, or a **time-delay element**.




555 TIMER - Astable Operation

- Astable Operation
 - A 555 timer connected to operate in the **astable mode** as a **free-running relaxation oscillator** (astable multivibrator) is shown in the figure.
 - Notice that the threshold input (**THRESH**) is now connected to the trigger input (**TRIG**).
 - The external components **R_1** , **R_2** , and **C_{ext}** form the timing circuit that sets the **frequency** of oscillation.
 - The $0.01\mu\text{F}$ capacitor connected to the control (**CONT**) input is strictly for decoupling and has no effect on the operation.

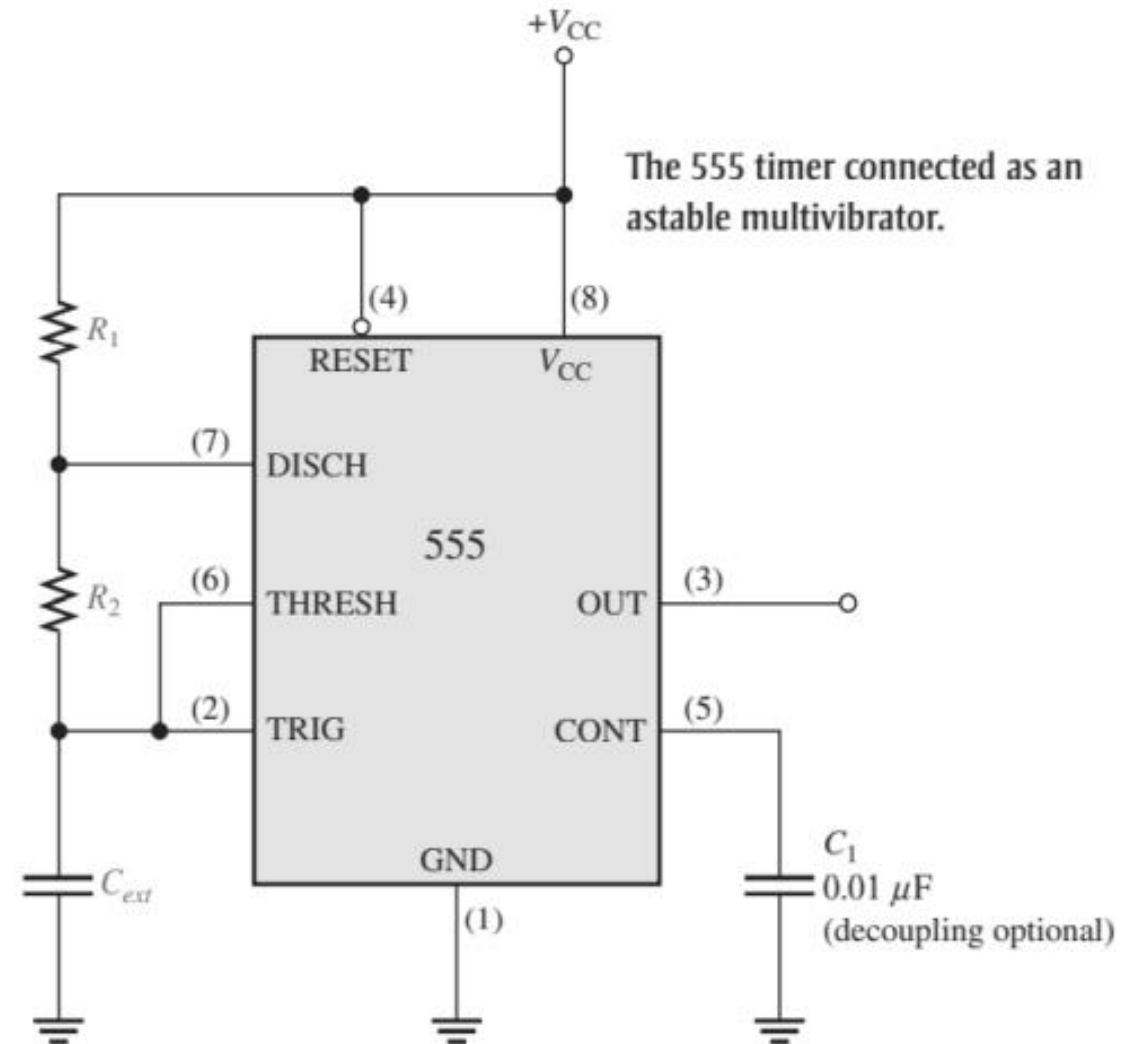


555 TIMER - Astable Operation

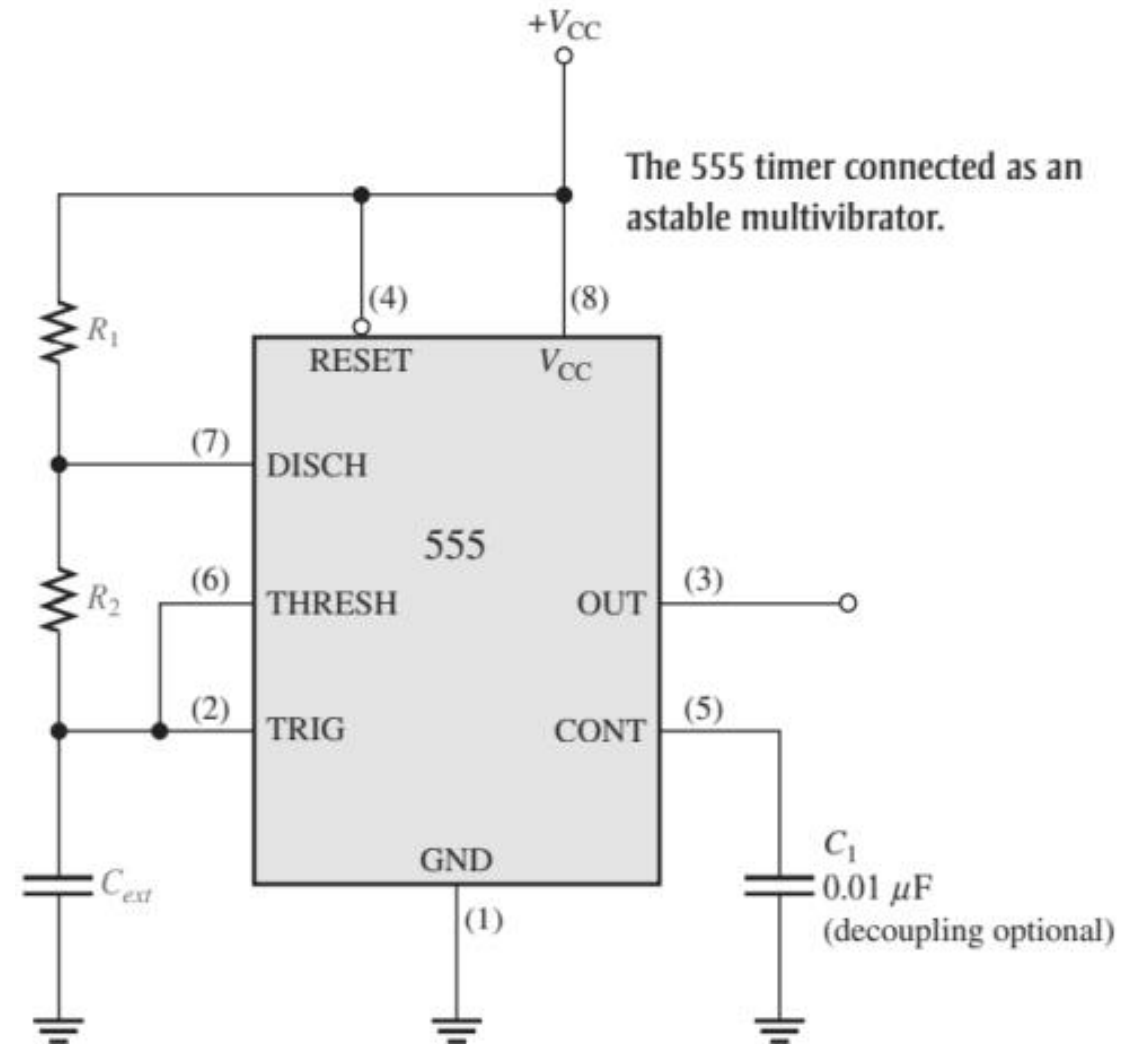- Astable Operation
 - **Decoupling capacitors** are used to isolate or decouple two circuits.
 - In other words, they **decouple AC signals from DC signals** or vice versa.
 - In case of input voltage drop, it provides adequate power to an IC to maintain the voltage level.




555 TIMER - Astable Operation

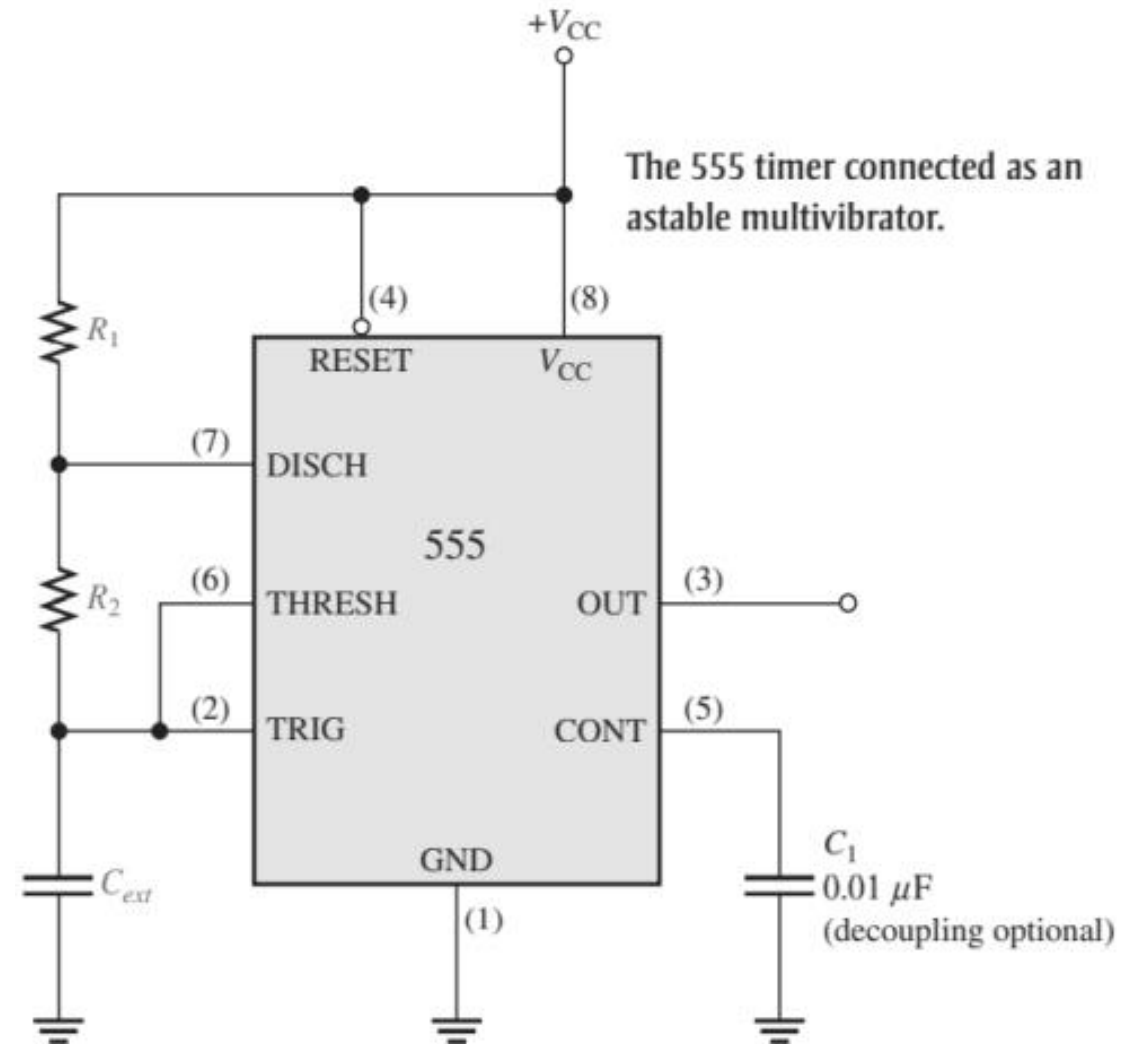- Initially, when the power is turned on, the capacitor C_{ext} is uncharged and thus the trigger voltage (pin 2) is at 0 V.
- This causes the output of the **lower comparator to be high** and the output of the **upper comparator to be low**, forcing the output of the flip-flop, and thus the base of Q_d low and keeping the **transistor off**.




555 TIMER - Astable Operation

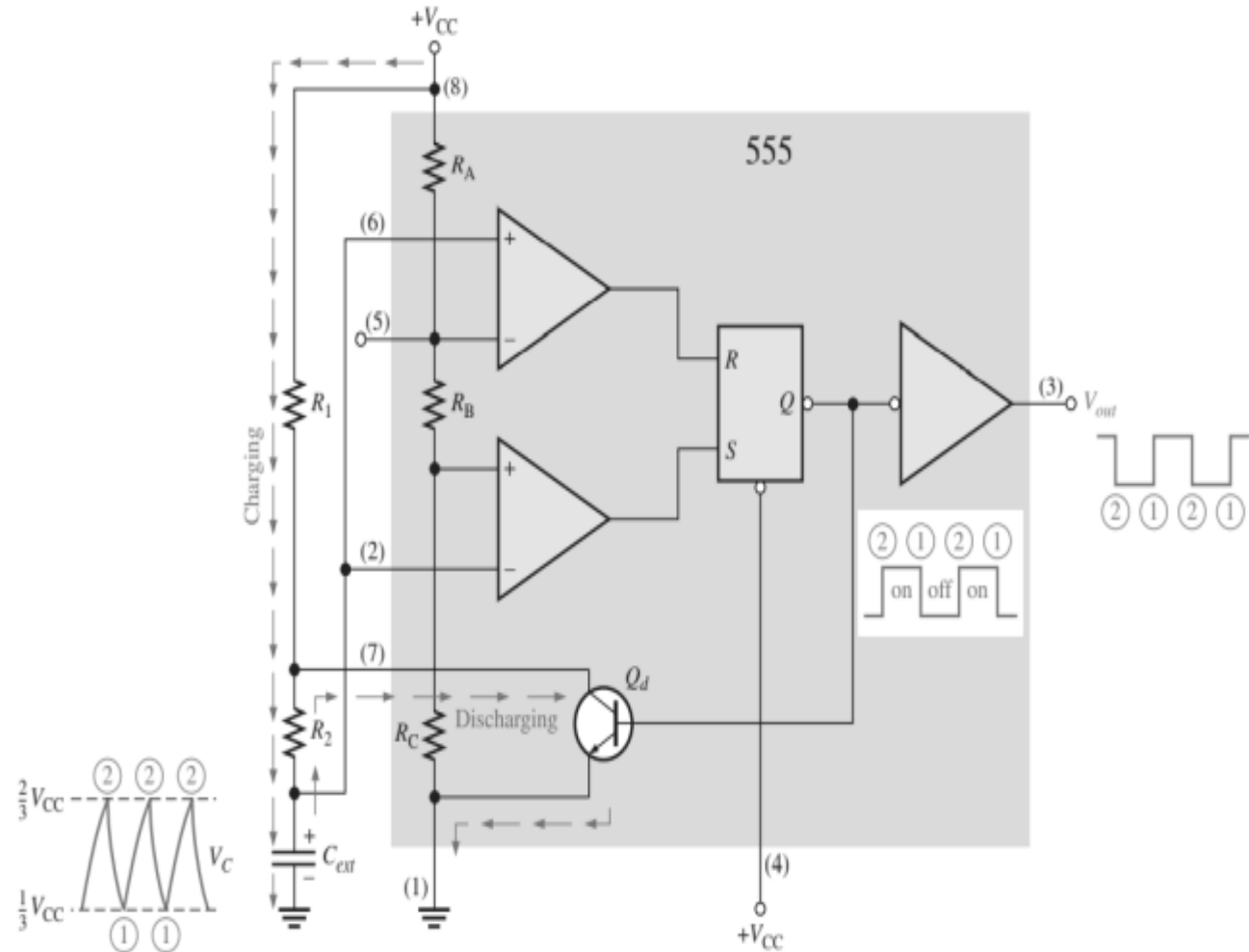- Now, *C_{ext}* begins charging through *R*₁ and *R*₂ as indicated in figure.
- When the capacitor voltage reaches $\frac{1}{3}V_{CC}$, the lower comparator switches to its low output state, and when the capacitor voltage reaches $\frac{2}{3}V_{CC}$, the upper comparator switches to its high output state.



555 TIMER - Astable Operation

- This resets the flip-flop, causes the base ***Qd* of to go high**, and turns on the transistor.
- This sequence creates a discharge path for the capacitor through R_2 and the transistor, as indicated.
- The capacitor now begins to discharge, causing the **upper comparator to go low**.
- At the point where the capacitor discharges down to $\frac{1}{3}V_{CC}$, the **lower comparator switches high**, setting the flip-flop, which makes the base of Q_d low and turns off the transistor.
- Another charging cycle begins, and the entire process repeats. The result is a **rectangular wave** output whose **duty cycle** depends on the values of **R_1 and R_2** .

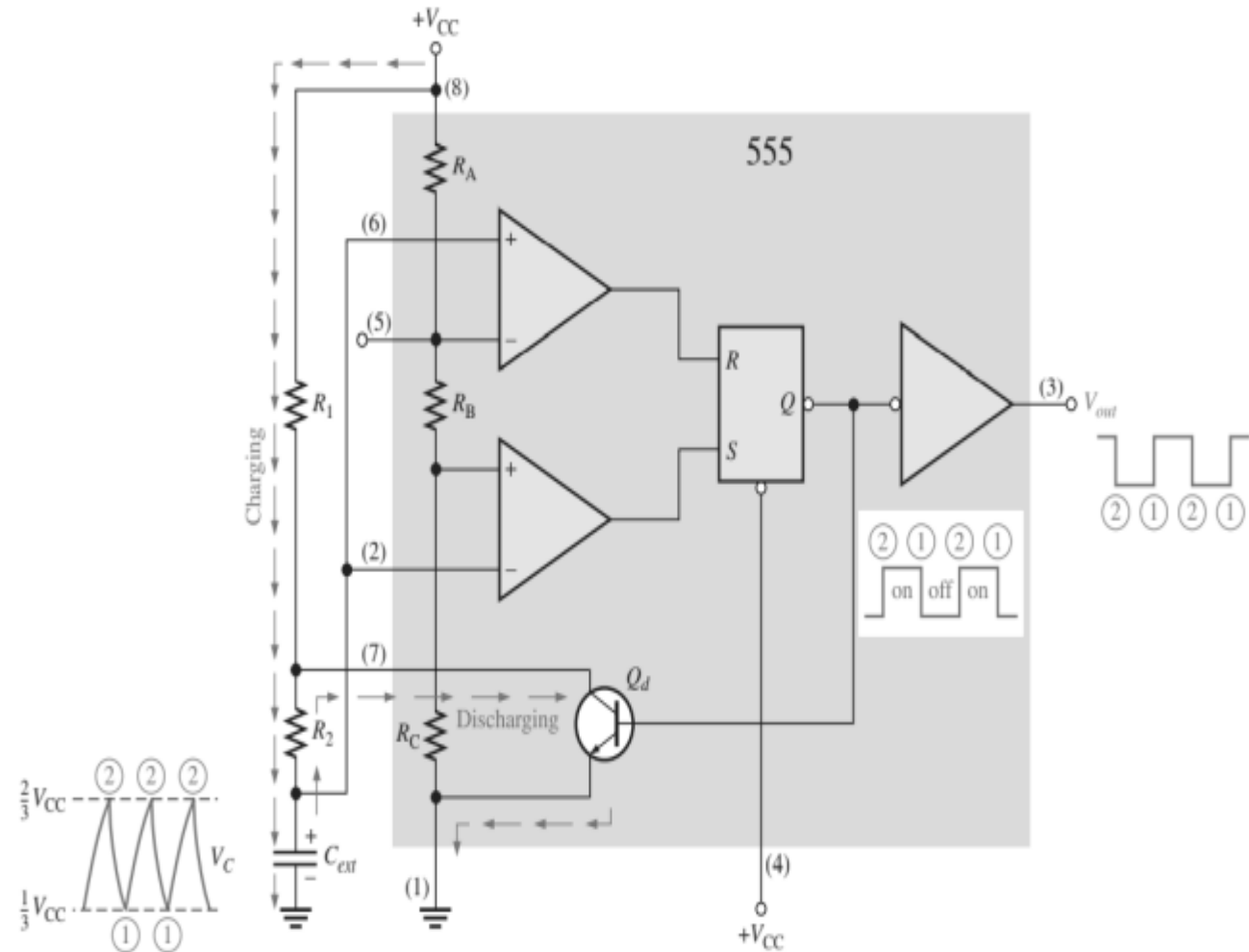


555 TIMER - Astable Operation

The frequency of oscillation is given by:

$$f_r = \frac{1.44}{(R_1 + 2R_2)C_{ext}}$$

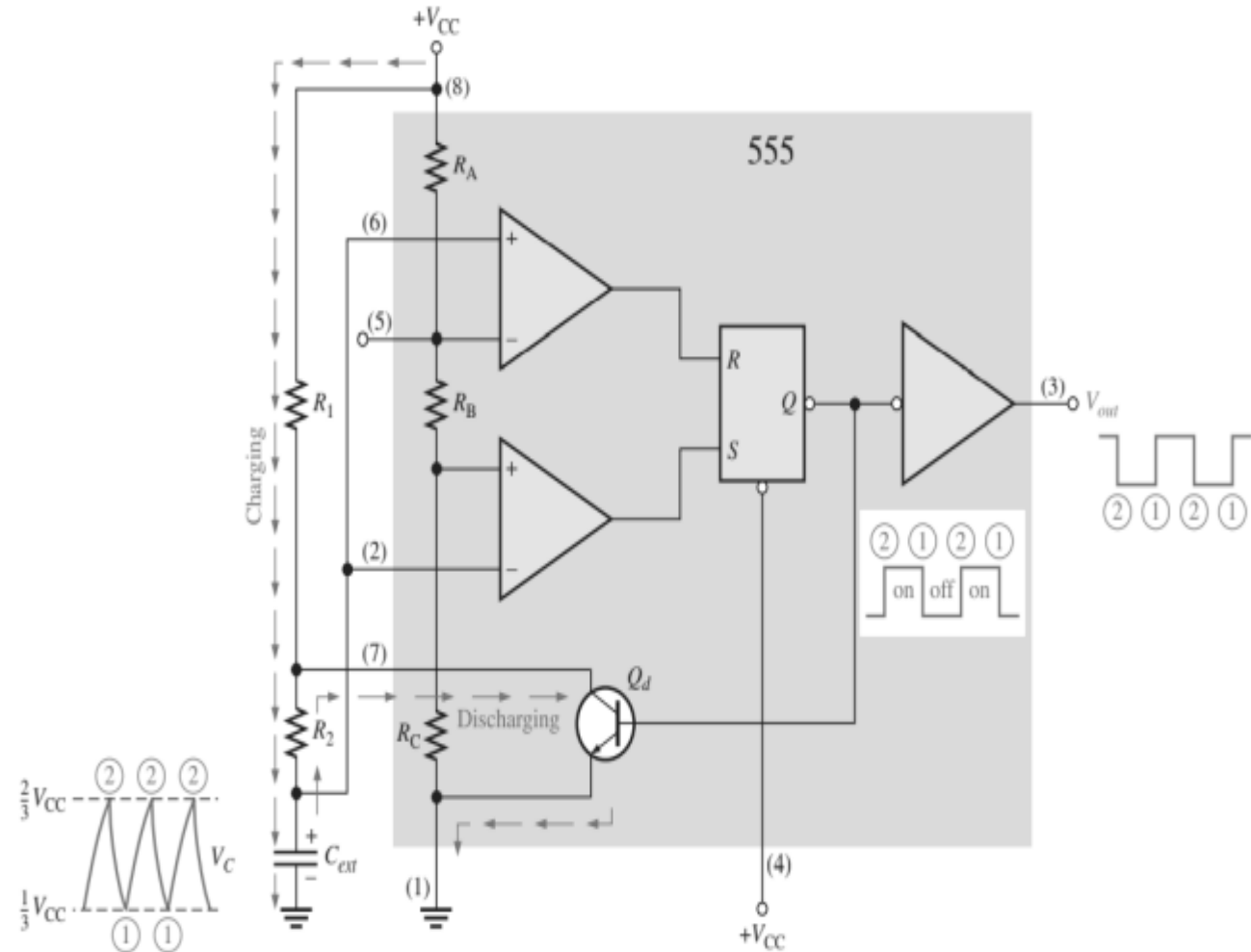
- By selecting R_1 and R_2 the duty cycle of the output can be adjusted.
- Since C_{ext} charges through $R_1 + R_2$ and discharges only through R_2 duty cycles approaching a minimum of 50 percent can be achieved if $R_2 \gg R_1$ so that the charging and discharging times are approximately equal.



555 TIMER - Astable Operation

- The time that the output is high (t_H) is how long it takes C_{ext} to charge from $\frac{1}{3}V_{CC}$ to $\frac{2}{3}V_{CC}$:
- The time that the output is low (t_L) is how long it takes C_{ext} to discharge from $\frac{2}{3}V_{CC}$ to $\frac{1}{3}V_{CC}$:
- The period, T , of the output waveform is the sum of t_H and t_L :
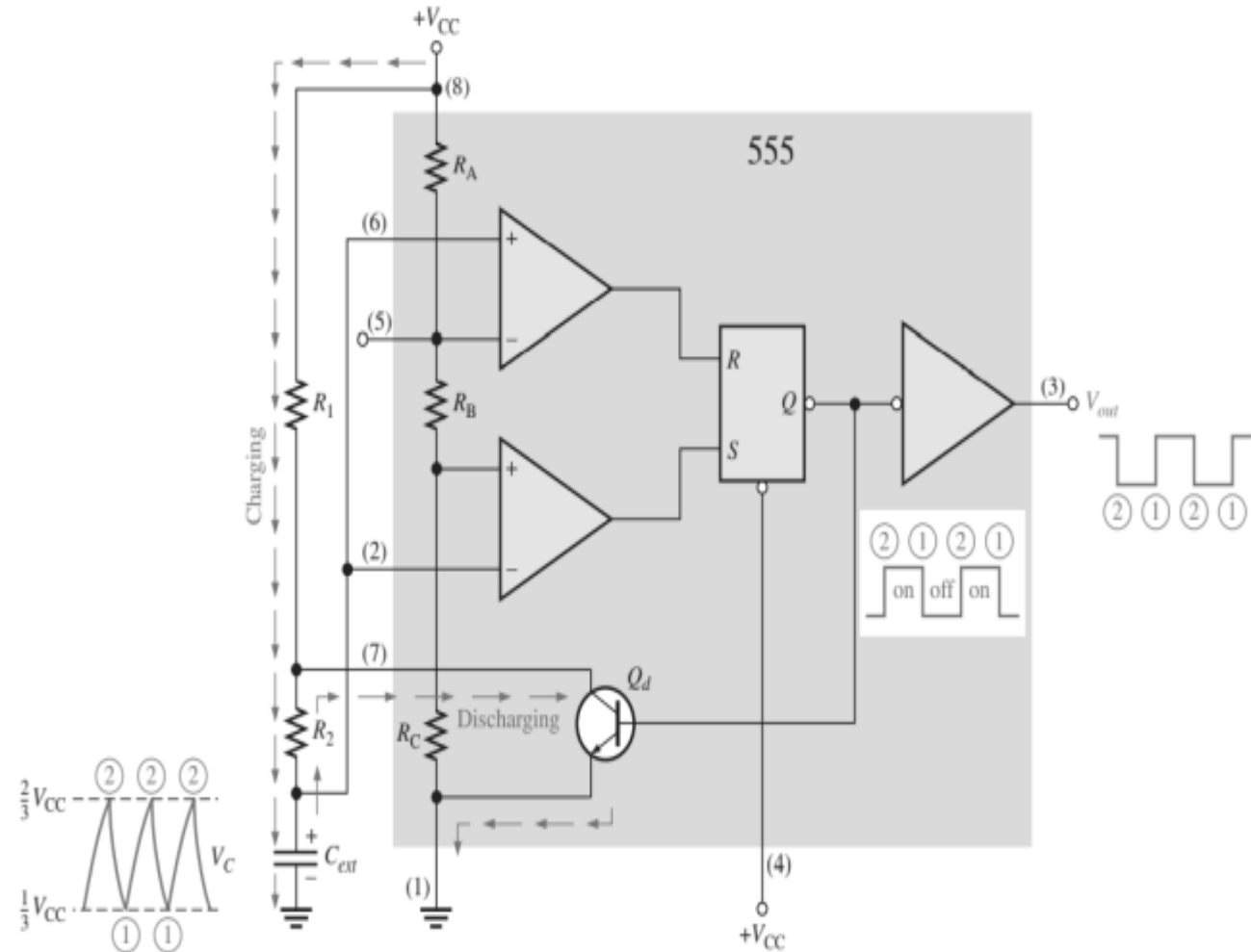
$$T = t_H + t_L = 0.694(R_1 + 2R_2)C_{ext}$$




555 TIMER - Astable Operation

- The percent duty cycle (D):

$$\text{Duty cycle} = \left(\frac{t_H}{T} \right) 100\% = \left(\frac{t_H}{t_H + t_L} \right) 100\%$$

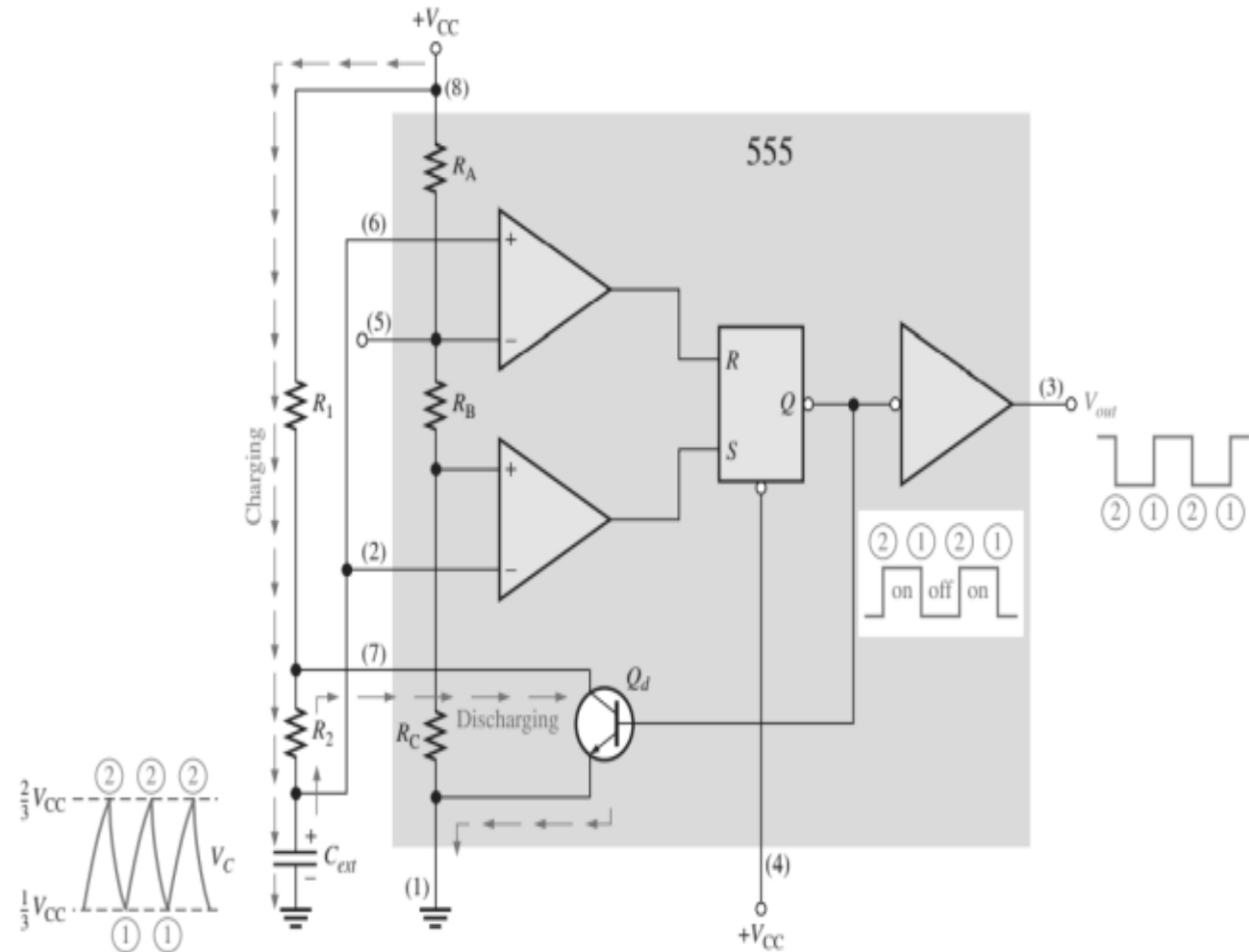
$$\text{Duty cycle} = \left(\frac{R_1 + R_2}{R_1 + 2R_2} \right) 100\%$$



555 TIMER - Astable Operation


- To achieve duty cycles of **less than 50 percent**, the circuit can be modified so that **C_{ext} charges through R_1 only** and **discharges through R_2** .
- This is achieved with a **diode, D_1** , placed as shown in the figure.
- The duty cycle can be made less than 50 percent by making **R_1 less than R_2** . Under this condition, the formulas for the frequency and percent duty cycle are (assuming an ideal diode)
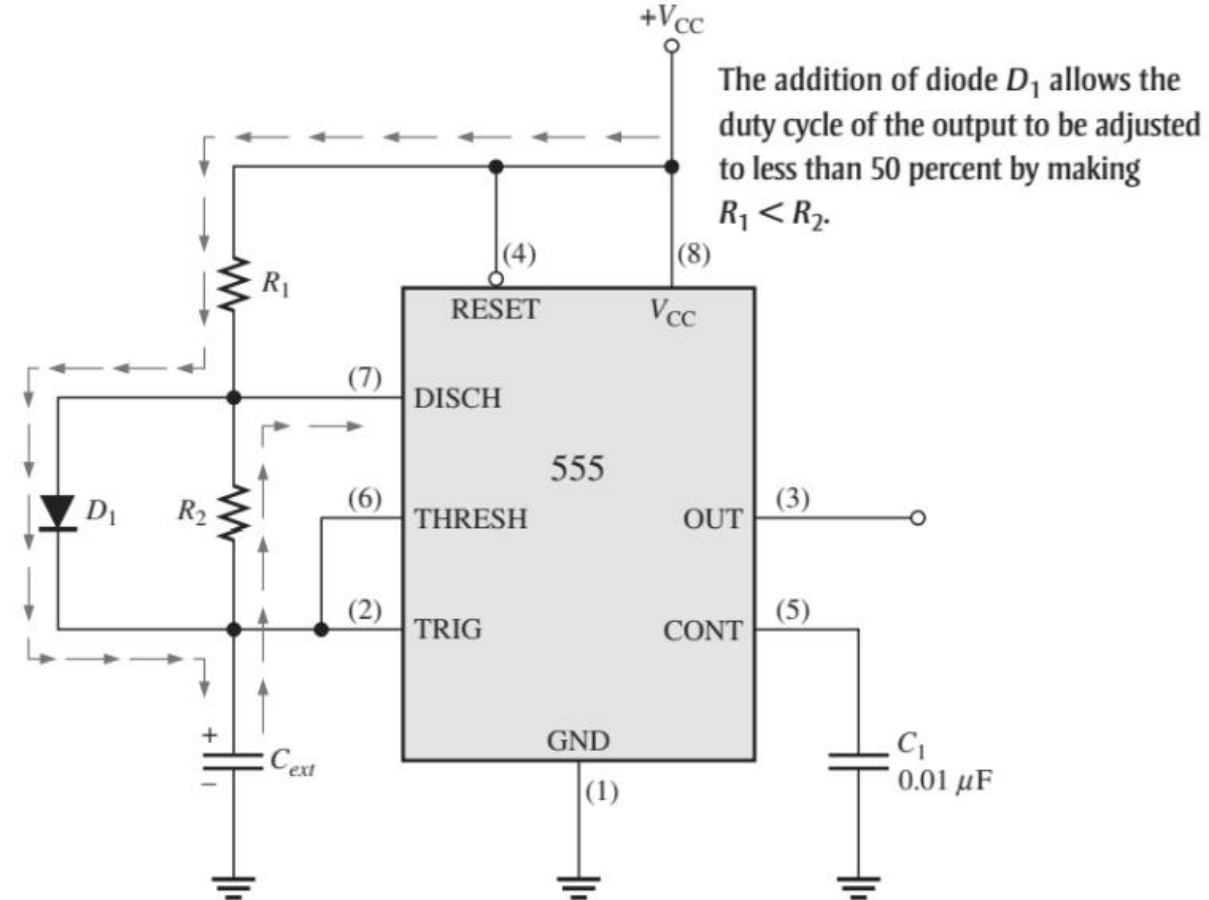
$$f_r \cong \frac{1.44}{(R_1 + R_2)C_{ext}}$$
$$\text{Duty cycle} = \left(\frac{R_1}{R_1 + 2R_2} \right) 100\%$$




555 TIMER - Voltage-Controlled Oscillator (VCO)

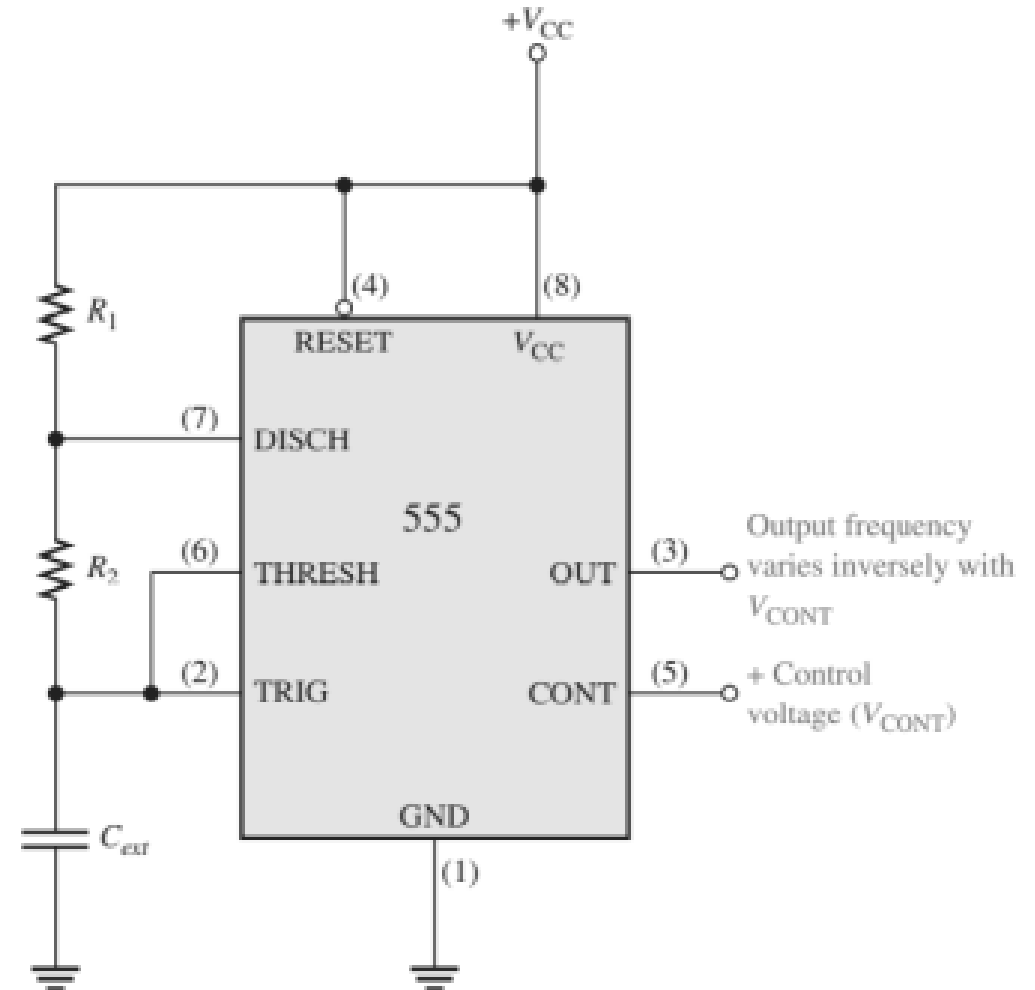- A 555 timer can be set up to operate as a **VCO** by using the same external connections as for astable operation, with the exception that a **variable control voltage is applied to the CONT input (pin 5)**, as indicated in the figure.



555 TIMER - Voltage-Controlled Oscillator (VCO)

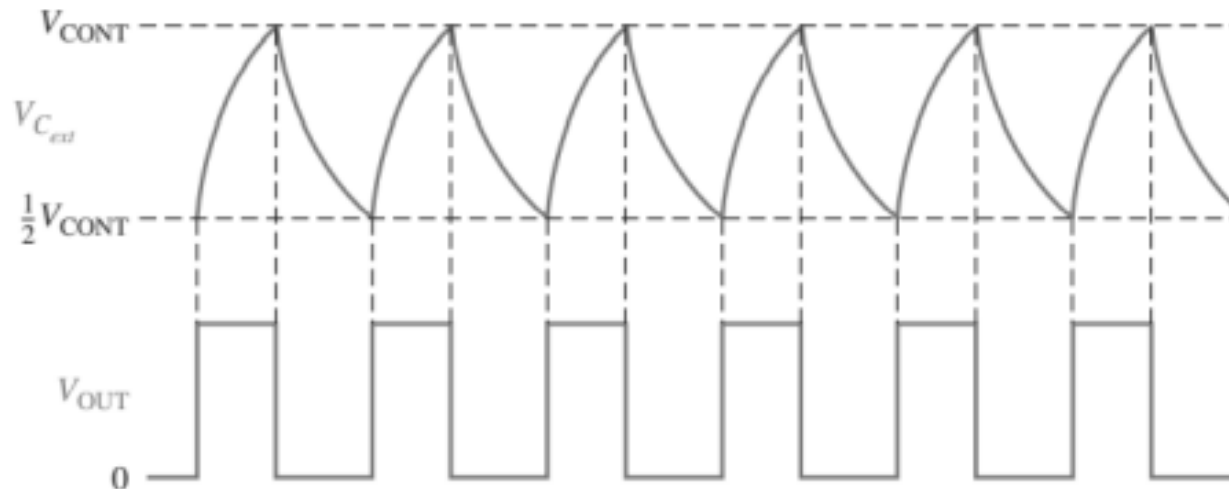
- As shown in the figure, the control voltage (V_{CONT}) changes the threshold values of $\frac{1}{3}V_{CC}$ and $\frac{2}{3}V_{CC}$ for the internal comparators.
- With the control voltage, the upper value is V_{CONT} and the lower value is $\frac{1}{2}V_{CONT}$.



The VCO output frequency varies inversely with V_{CONT} because the charging and discharging time of C_{ext} is directly dependent on the control voltage.

555 TIMER - Voltage-Controlled Oscillator (VCO)

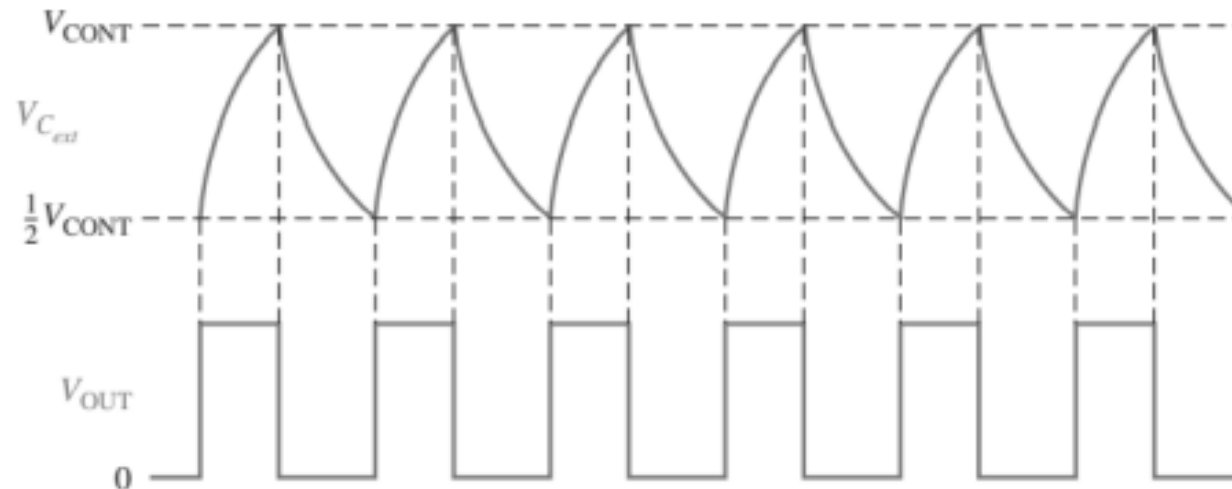
- When the control voltage is varied, the output frequency also varies.
- An **increase in V_{CONT} increases the charging and discharging time** of the external capacitor and **causes the frequency to decrease**.
- A **decrease in V_{CONT} decreases the charging and discharging time** of the capacitor and **causes the frequency to increase**.



The VCO output frequency varies inversely with V_{CONT} because the charging and discharging time of C_{ext} is directly dependent on the control voltage.

555 TIMER - Voltage-Controlled Oscillator (VCO)

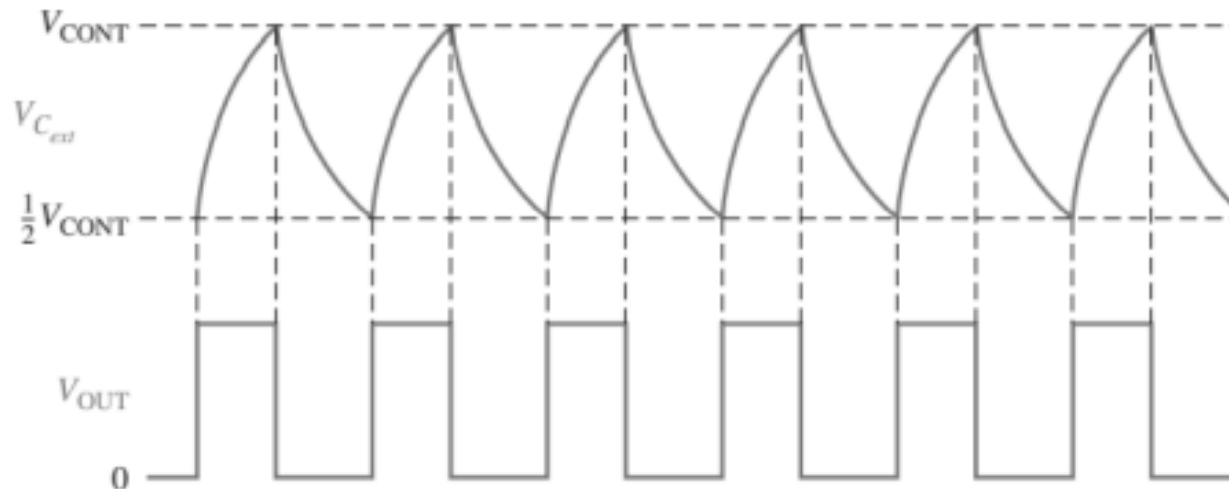- An interesting application of the VCO is in **phase-locked loops**, which are used in various types of communication receivers to **track variations in the frequency of incoming signals**.



The VCO output frequency varies inversely with V_{CONT} because the charging and discharging time of C_{ext} is directly dependent on the control voltage.

Problem Solving


- Determine the frequency of oscillation of the circuit in the figure; and to what value must R_1 be changed to make the frequency 20 kHz?

$$f_r = \frac{1}{4R_1C} \left(\frac{R_2}{R_3} \right)$$

Ans.

$$f_r = 8.25 \text{ kHz}$$

$$R_1 = 4.125 \text{ k}\Omega$$

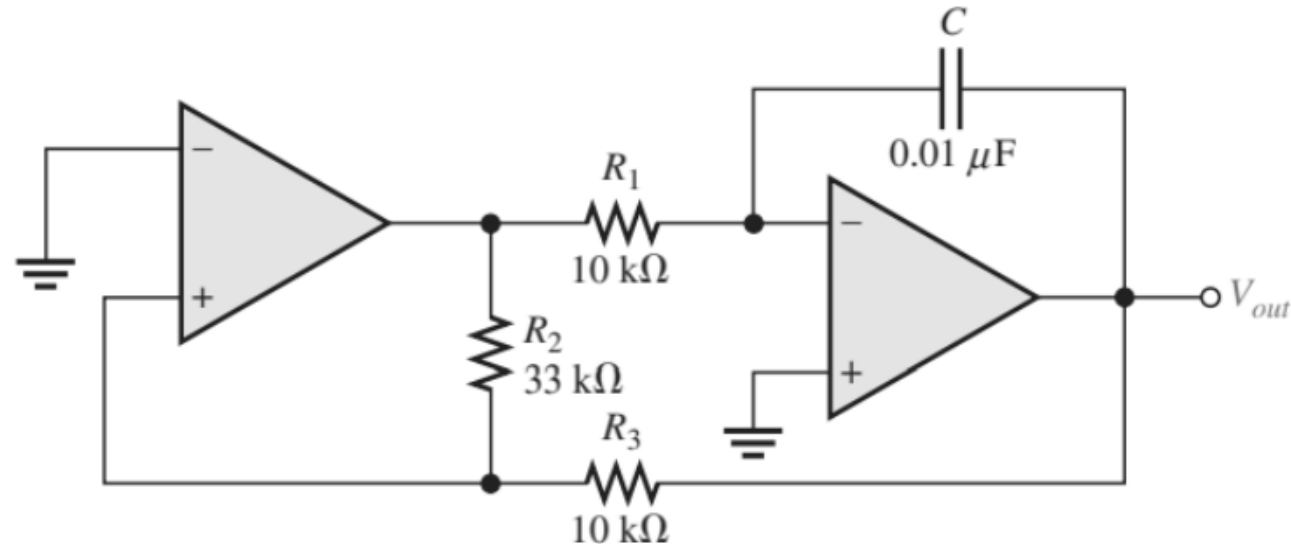

Problem Solving

- A 555 timer configured to run in the astable mode (oscillator) is shown in the figure. Determine the frequency of the output and the duty cycle.

$$f_r = \frac{1.44}{(R_1 + 2R_2)C_{ext}} \quad \text{Duty cycle} = \left(\frac{t_H}{T}\right) 100\% = \left(\frac{t_H}{t_H + t_L}\right) 100\%$$
$$\text{Duty cycle} = \left(\frac{R_1 + R_2}{R_1 + 2R_2}\right) 100\%$$

Ans.

$$f = 5.64 \text{ kHz}$$

$$D = 59.48\%$$

