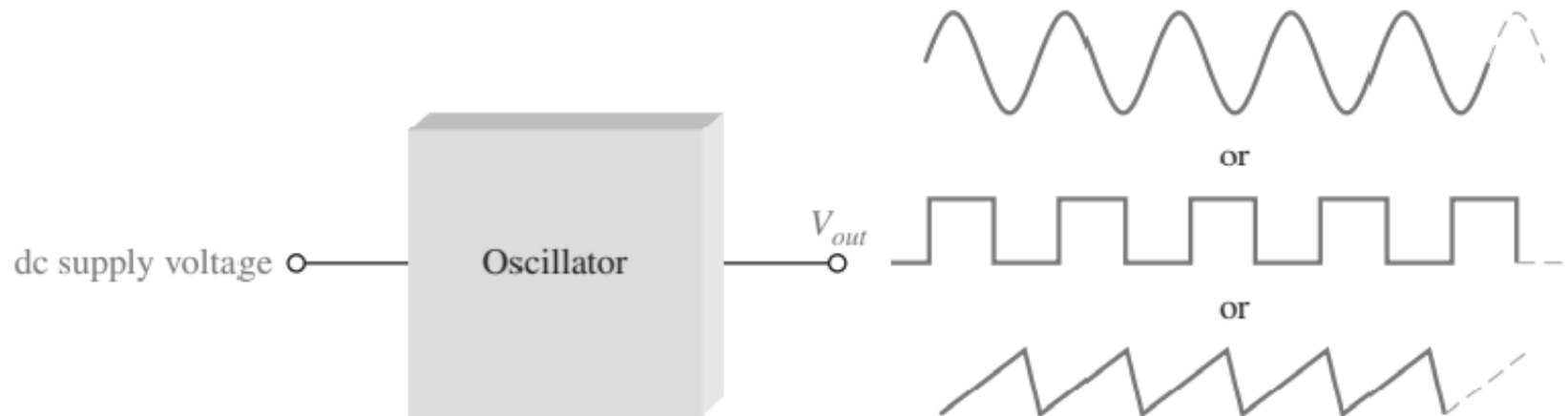


Oscillators

Oscillators

- **Oscillators** are electronic circuits that generate an output signal **without** the necessity of an **input signal**.
- Converts electrical energy from the **dc** power supply to **periodic waveforms**.
- They are used as signal sources in all sorts of applications.
- Different types of oscillators produce various types of outputs including sine waves, square waves, triangular waves, and sawtooth waves.
- Sinusoidal oscillator operation is based on the principle of **positive feedback**, where a portion of the output signal is fed back to the input in a way that causes it to reinforce itself and thus sustain a continuous output signal.

Oscillators



The basic oscillator concept showing three common types of output waveforms: sine wave, square wave, and sawtooth.


Oscillators

Two major classifications for oscillators:

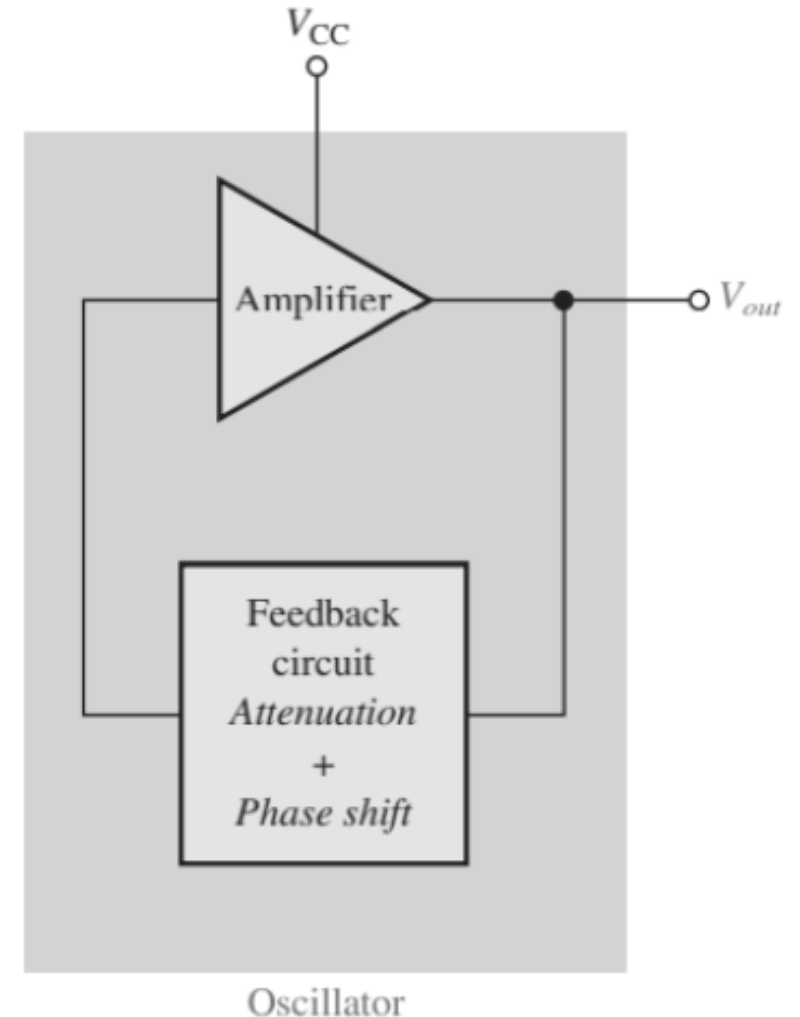- a) Feedback oscillators
- b) Relaxation oscillators

Feedback Oscillators

- A type of oscillator which **returns a fraction of the output** signal to the input with **no net phase shift**, resulting in a reinforcement of the output signal.
- After oscillations are started, the loop gain is **maintained at 1.0** to maintain oscillations.
- A feedback oscillator consists of an amplifier for gain (either a discrete transistor or an op-amp) and a positive feedback circuit that produces phase shift and provides attenuation.




Relaxation Oscillators

- A type of oscillator that uses an RC timing circuit to generate a waveform, instead of feedback, that is generally a square wave or other non-sinusoidal waveform.
- Typically, a relaxation oscillator uses a Schmitt trigger or other device that changes states to alternately charge and discharge a capacitor through a resistor.



Positive feedback

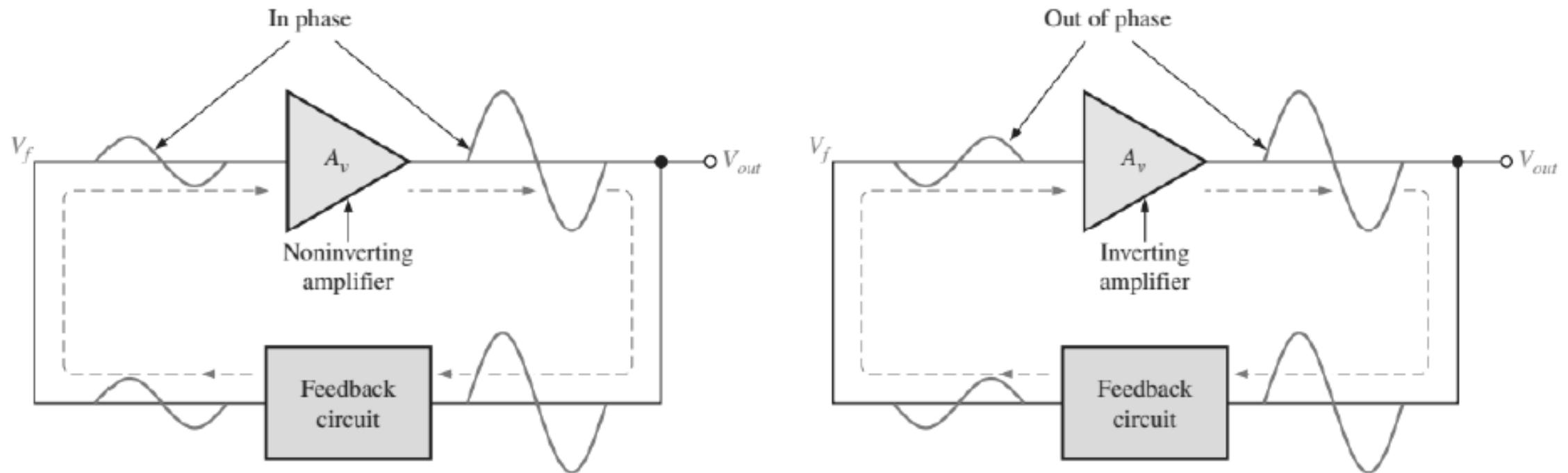- Characterized by the condition wherein a portion of the output voltage of an amplifier is **fed back to the input with no net phase shift**, resulting in a reinforcement of the output signal.



Conditions for Oscillation

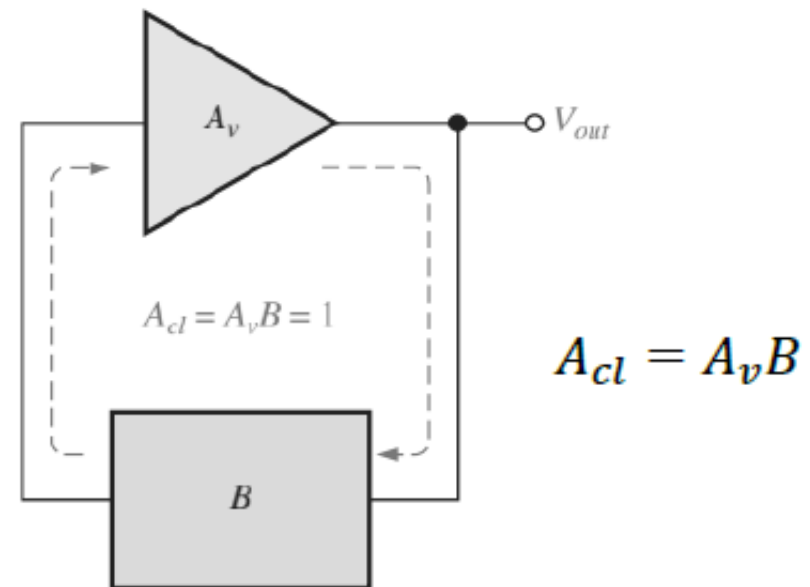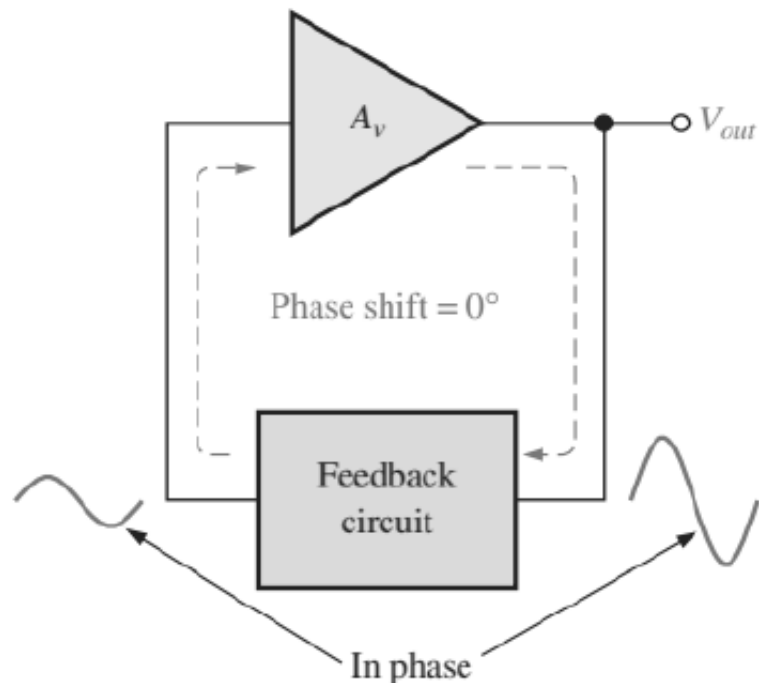
- Two conditions are required for a sustained state of oscillation:
 - 1) The **phase shift** around the feedback loop must be effectively **0°** .
 - 2) The **voltage gain** A_{cl} , around the **closed feedback loop** (loop gain) must equal 1 (unity).



Start-Up Conditions to Oscillate

For oscillation to begin, the **voltage gain** around the positive **feedback loop** **must be greater than 1** so that the amplitude of the output can build up to a desired level.

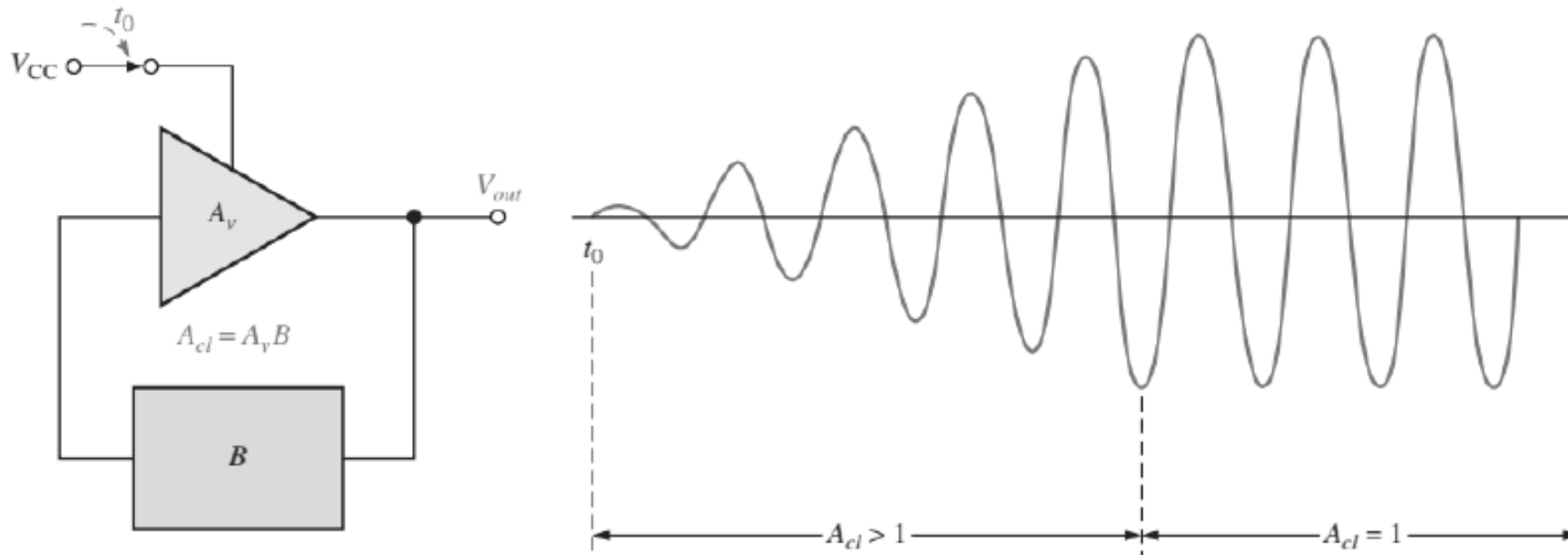The gain must then decrease to 1 so that the output stays at the desired level and oscillation is sustained.



Oscillators with RC Feedback Circuits

Three types of feedback oscillators that use RC circuits:

- 1) Wien-bridge oscillator
- 2) Phase-shift oscillator
- 3) Twin-T oscillator

Wien Bridge Oscillator

The standard oscillator circuit for all freq. in the range of 10 Hz to about 1 MHz.

It is the most frequently used type of audio oscillator as the output is free from circuit fluctuations and ambient temp.


Frequency of Oscillations (f_r):

$$f_r = \frac{1}{2\pi\sqrt{R_1C_1R_2C_2}}$$

If $R_1 = R_2 = R$ and $C_1 = C_2 = C$

Then,

$$f_r = \frac{1}{2\pi RC}$$


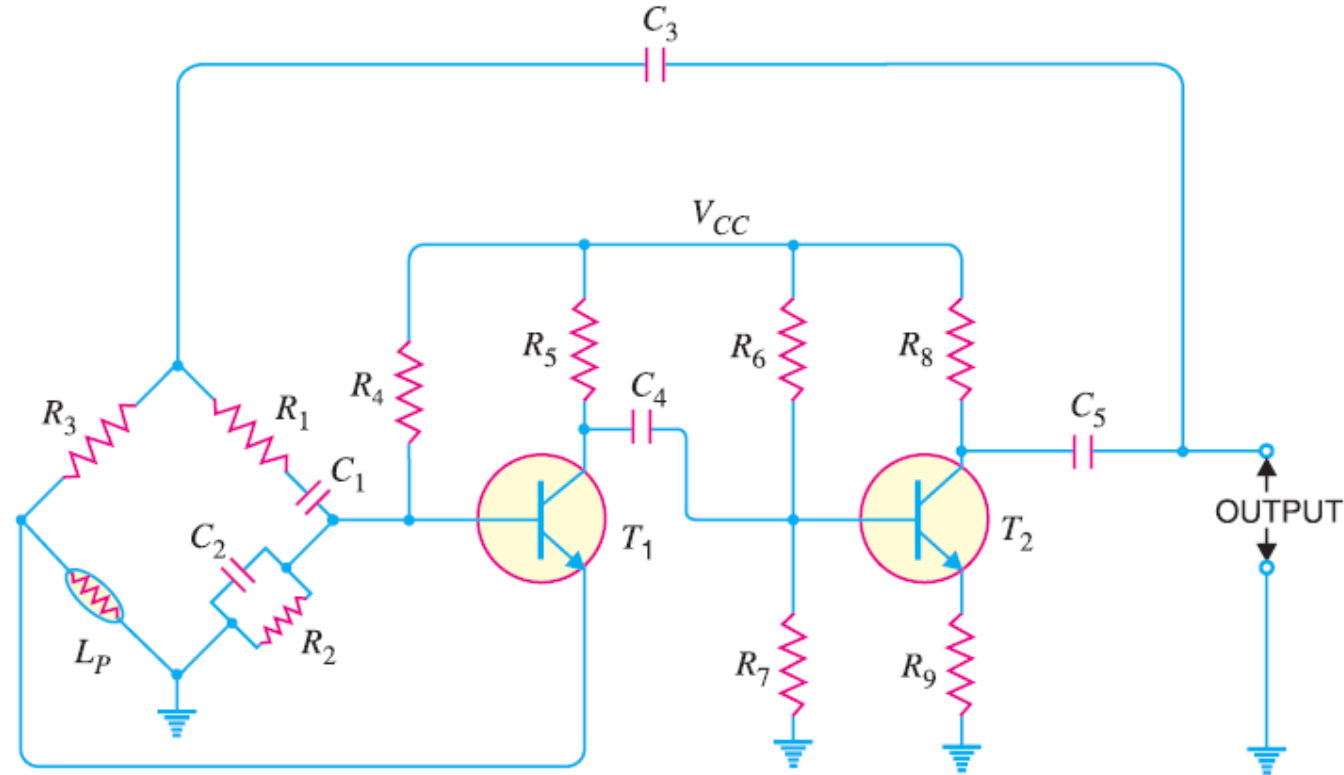


Wien-Bridge Oscillator

A fundamental part of the Wien-bridge oscillator is a **lead-lag circuit** like that shown in the figure.

R_1 and C_1 together form the **lag portion** of the circuit; R_2 and C_2 form the **lead portion**.

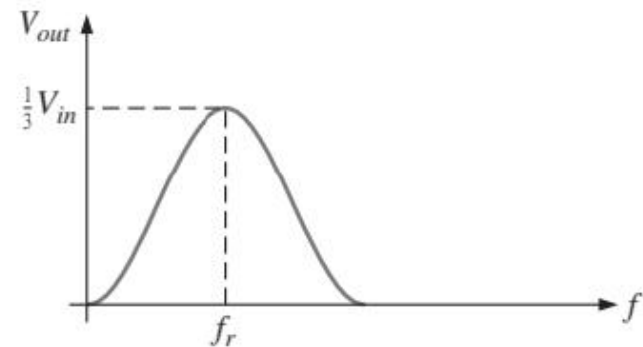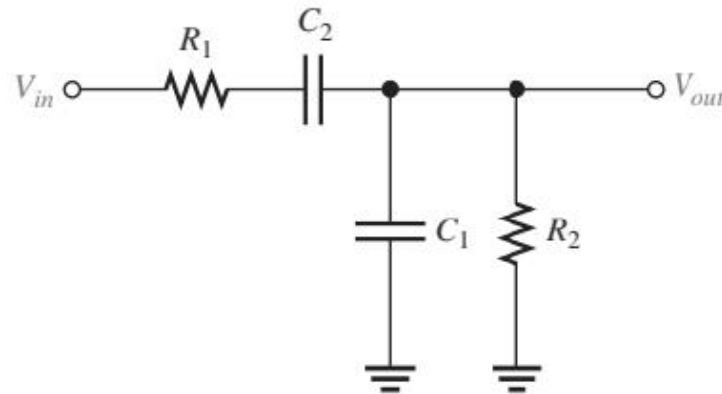The lead-lag circuit has a resonant frequency, f_r , at which the phase shift through the circuit is 0° and the **attenuation is $1/3$** . Below f_r , the lead circuit dominates and the output leads the input. Above f_r , the lag circuit dominates and the output lags the input.



Wien Bridge Oscillator

Advantages

- It gives constant output.
- The circuit works quite easily.
- The overall gain is high because of two transistors.
- The frequency of oscillations can be easily changed by using a potentiometer.

Disadvantages

- The circuit requires two transistors and a large number of components.
- It cannot generate very high frequencies.

Example

In the Wien bridge oscillator shown in Fig. 14.18, $R_1 = R_2 = 220\text{ k}\Omega$ and $C_1 = C_2 = 250\text{ pF}$. Determine the frequency of oscillations.

Ans.

2892 Hz

Phase Shift Oscillators

The phase shift network consists of **three** sections **R_1C_1 , R_2C_2 and R_3C_3** . At some particular frequency f_r , the phase shift in each RC section is 60° , total of 180° .

Frequency of Oscillations (f_r):


$$f_r = \frac{1}{2\pi RC\sqrt{6}}$$

Where:

$$R_1 = R_2 = R_3 = R ; C_1 = C_2 = C_3 = C$$

Feedback Fraction (β):
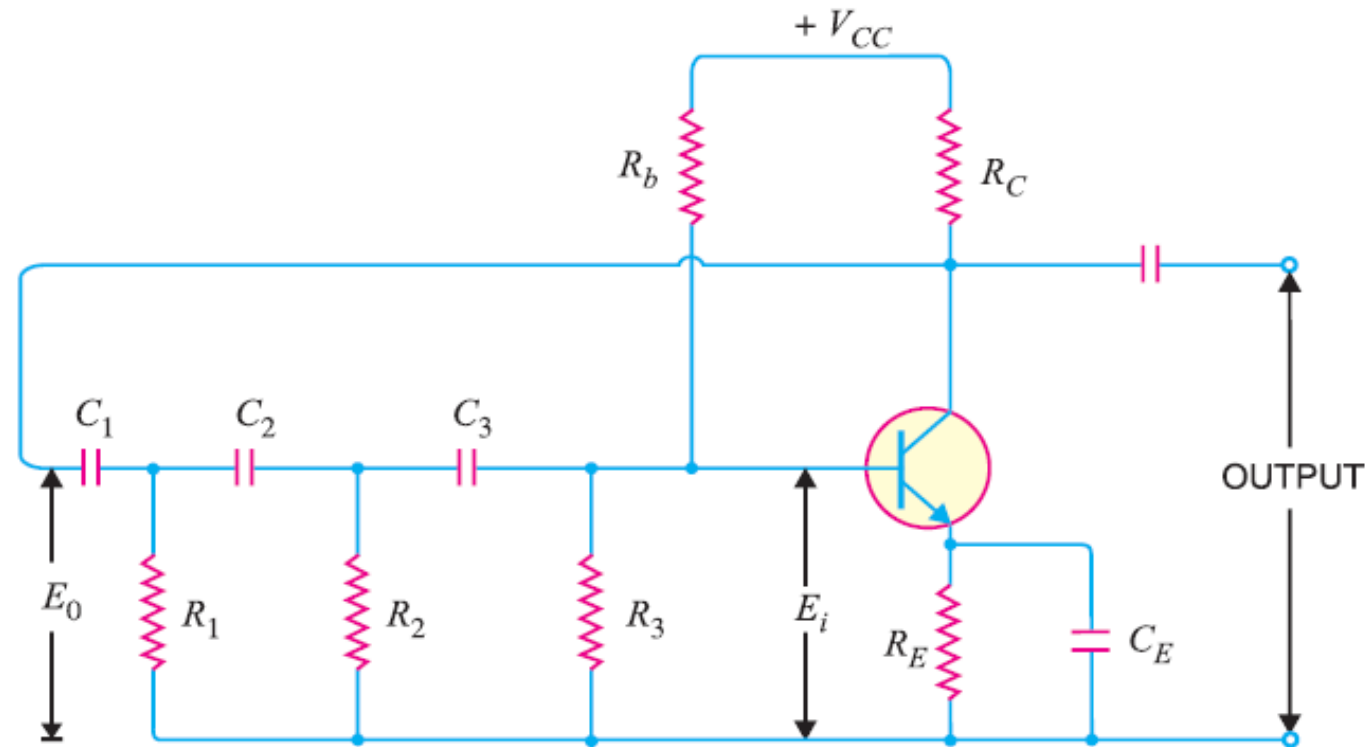
$$\beta = \frac{V_f}{V_0} = \frac{E_i}{E_0} = \frac{1}{29}$$



Phase Shift Oscillators

Advantages

- It does not require transformers or inductors.
- It can be used to produce very low frequencies.
- The circuit provides good frequency stability.

Disadvantages

- It is difficult for the circuit to start oscillations as the feedback is generally small.
- The circuit gives small output.

Example

In a phase shift oscillator, $R_1 = R_2 = R_3 = 1\text{M}\Omega$ and $C_1 = C_2 = C_3 = 68\text{ pF}$.
At what frequency does the circuit oscillate ?

Ans.

954 Hz

Example

A phase shift oscillator uses 5 pF capacitors. Find the value of R to produce a frequency of 800 kHz.

Ans.

16.2 k Ω

Twin-T Oscillator



It is called the twin-T because of **the two T-type RC filters** used in the feedback loop.

One of the twin-T filters has a **low-pass response**, and the other has a **high-pass response**.

The combined parallel filters produce a band-stop or notch response with a center frequency equal to the desired frequency of oscillation, f_r .


Oscillation cannot occur at frequencies above or below f_r because of the **negative feedback through the filters**.

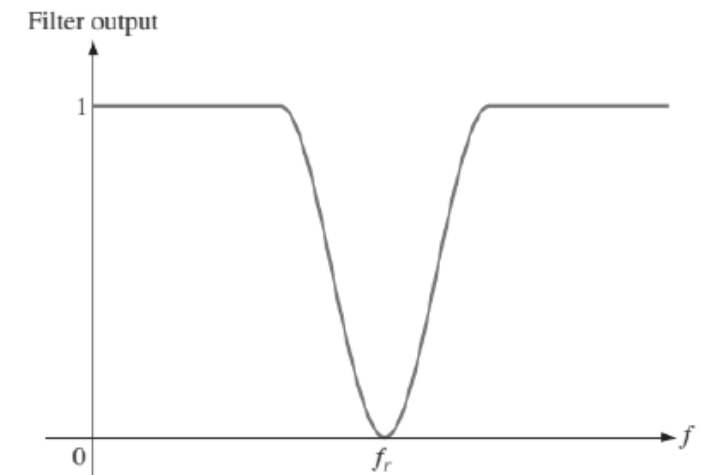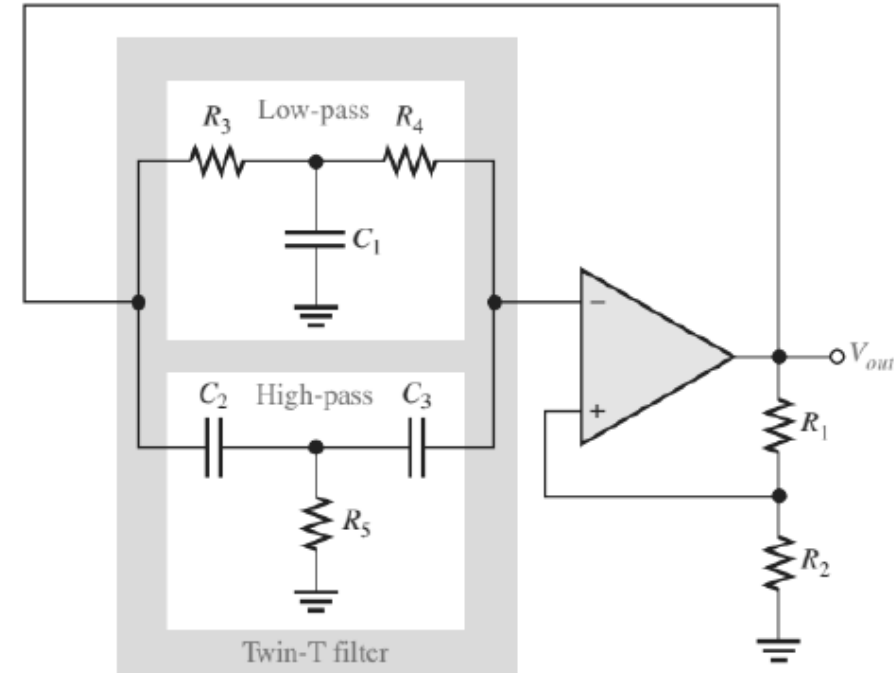At f_r , however, there is negligible negative feedback; thus, the positive feedback through the voltage divider (R_1 and R_2) allows the circuit to oscillate.




Twin-T Oscillator

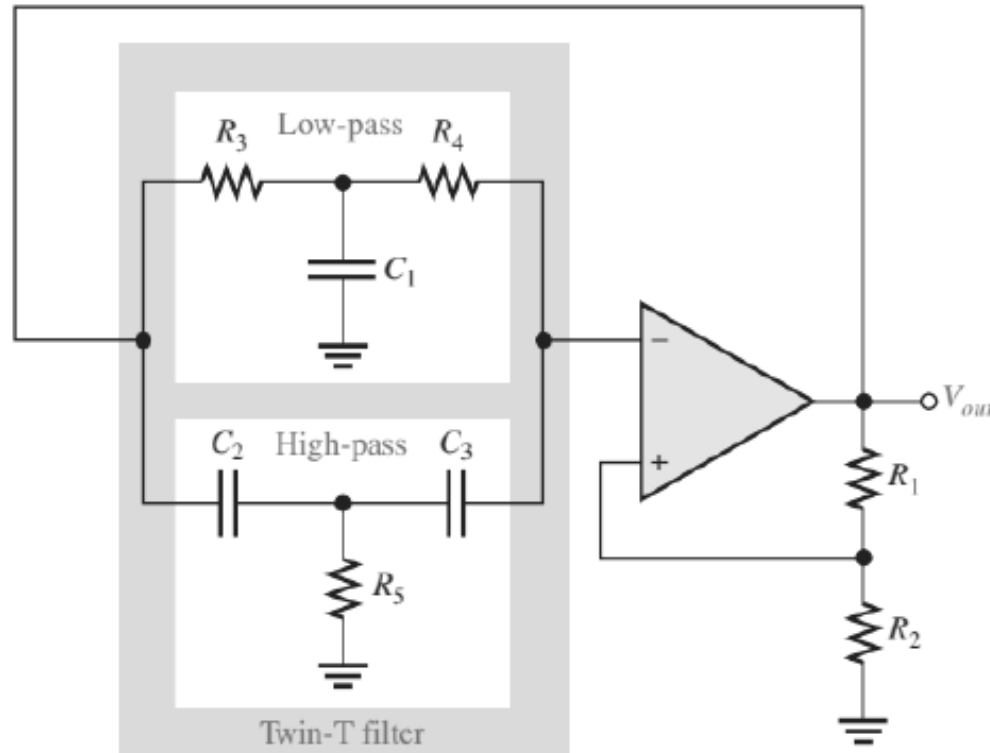- It is called the twin-T because of **the two T-type RC filters** used in the feedback loop.
- One of the twin-T filters has a **low-pass response**, and the other has a **high-pass response**.



(a) Oscillator circuit

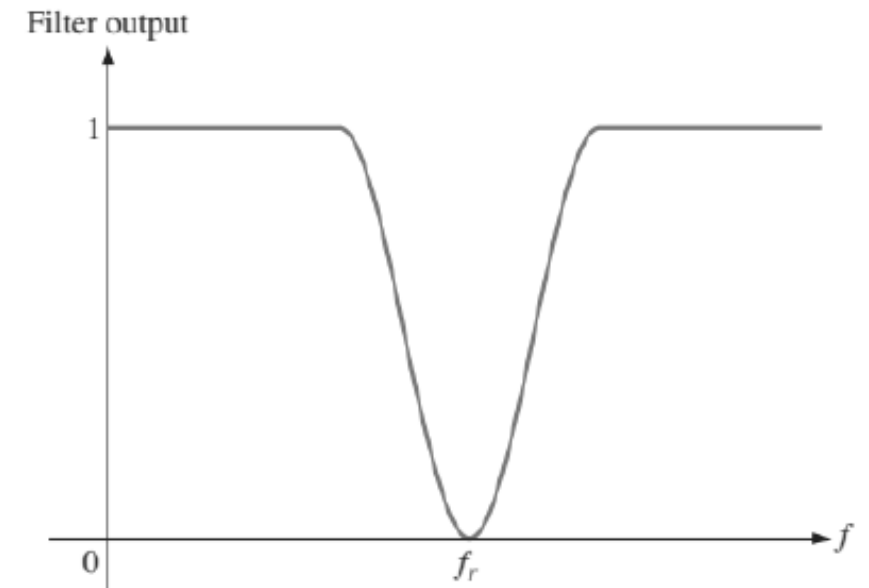

(b) Twin-T filter's frequency response curve

Twin-T Oscillator

- The combined parallel filters produce a band-stop or notch response with a center frequency equal to the desired frequency of oscillation, f_r .
- Oscillation cannot occur at frequencies above or below f_r because of the **negative feedback through the filters**.
- At f_r , however, there is **negligible negative feedback**; thus, the positive feedback through the voltage divider (R_1 and R_2) allows the circuit to